





Filters

- What is a filter
- Passive filters
- Some common filters

What are filters?

- **Filters** are electronic circuits which perform signal processing functions, specifically intended to remove unwanted signal components and/or enhance wanted ones.
- **Common types of filters:**
 - *Low-pass*: deliver low frequencies and eliminate high frequencies
 - *High-pass*: send on high frequencies and reject low frequencies
 - *Band-pass*: pass some particular range of frequencies, discard other frequencies outside that band
 - *Band-rejection*: stop a range of frequencies and pass all other frequencies (e.g., a special case is a *notch* filter)

Bode Plots of Common Filters

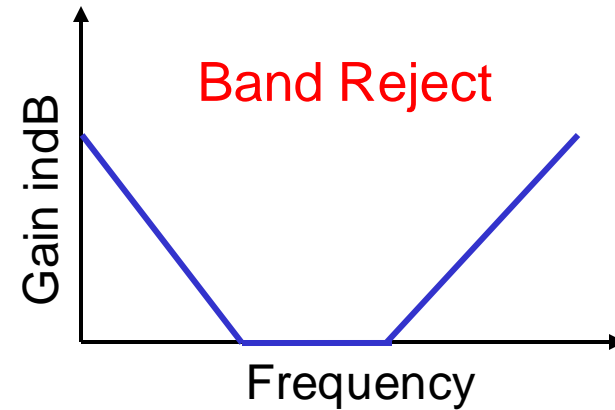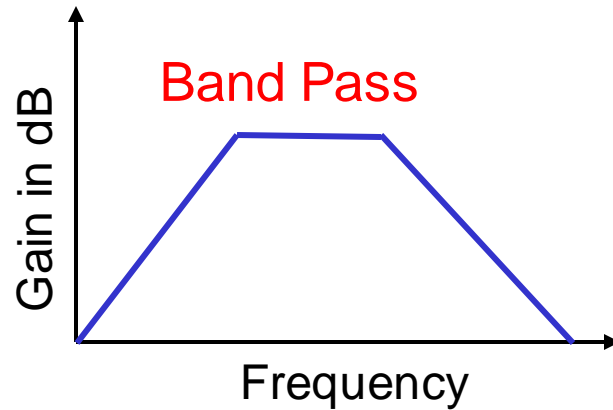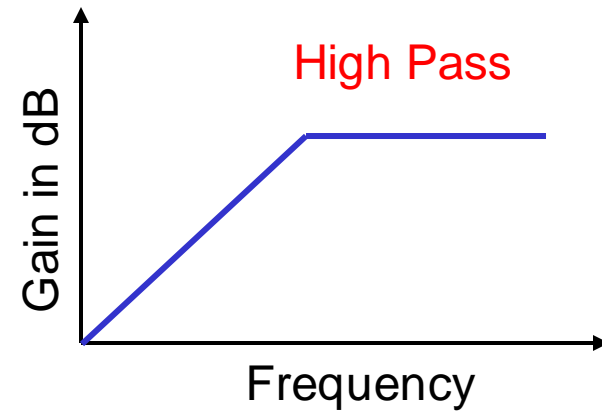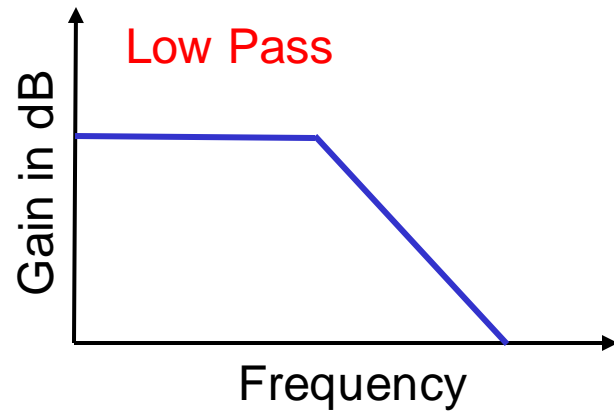

Passive vs. Active filters

- **Passive filters:** RLC components only, but gain < 1
- **Active filters:** op-amps with RC elements, and gain > 1

$$\text{Gain} = V_{\text{out}}/V_{\text{in}}$$

$$\text{Gain (in Decibel)} = 20 \log_{10}(V_{\text{out}}/V_{\text{in}})$$


$$* -3 \text{ dB} = 20 \log_{10}(0.707)$$

Passive Filters

- *Passive filters* use R , L , C elements to achieve the desired filter


Some Technical Terms:

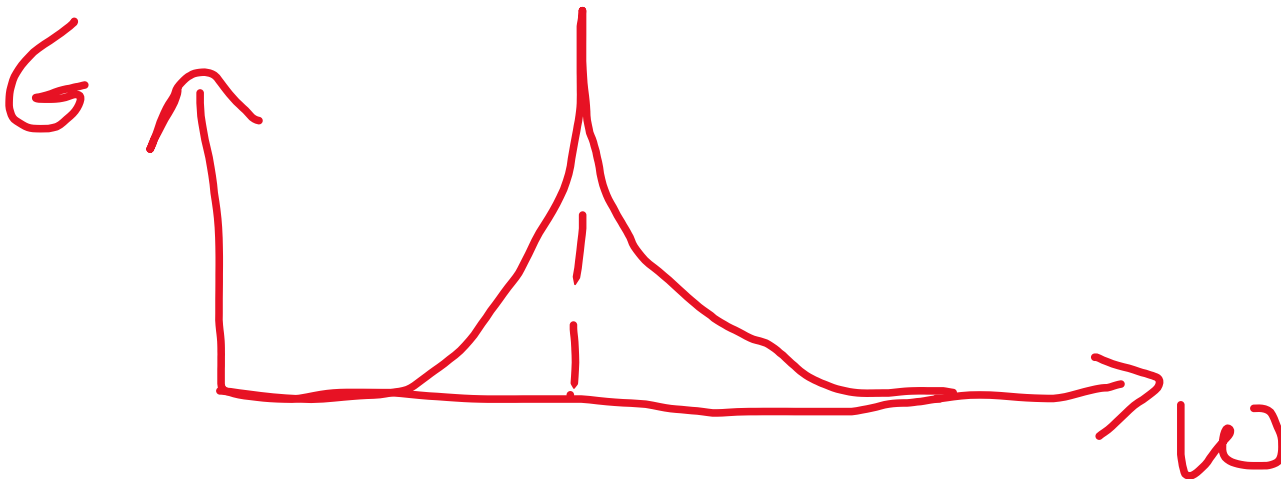- The *half-power frequency* is the same as the *break frequency* (or *corner frequency*) and is located at the frequency where the magnitude is $1/\sqrt{2}$ of its maximum value
- The *resonance frequency*, ω_0 , is also referred to as the *center frequency*



LOW-PASS FILTER

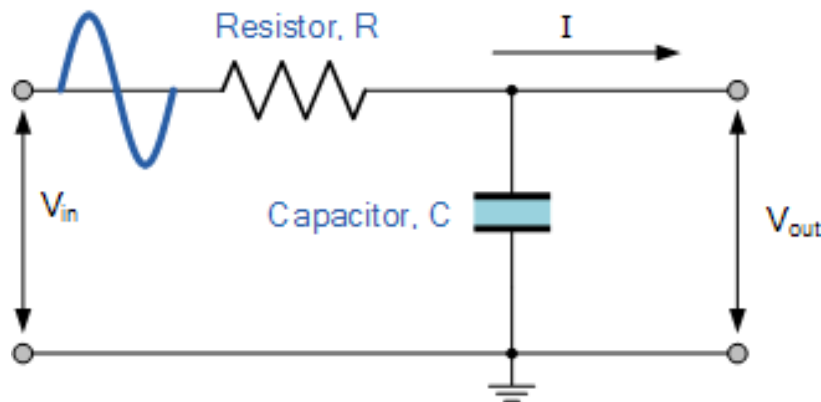- A low-pass filter allows for easy passage of low-frequency signals from source to load, and difficult passage of high-frequency signals.
- * The cutoff frequency for a low-pass filter is that frequency at which the output (load) voltage equals 70.7% of the input (source) voltage. Above the cutoff frequency, the output voltage is lower than 70.7% of the input, and vice versa.



First order low pass filter

$$V_o = V_c$$

$$V_o = \frac{X_c}{R + X_c} \cdot V_{in}$$

Cutoff freq. is also known as 3-dB frequency. Because gain at cutoff freq. is -3dB .

Cut-off Frequency and Phase Shift

$$f_c = \frac{1}{2\pi RC}$$

$$\text{Phase Shift } \phi = -\arctan(2\pi fRC)$$


$$\phi = -\tan^{-1}(\omega RC)$$

$$\omega=0 \Rightarrow -\tan^{-1}(0) = 0^\circ$$

$$\omega=\omega_c \Rightarrow -\tan^{-1}(1) = -45^\circ$$

$$\omega=\infty \Rightarrow -\tan^{-1}(\infty) = -90^\circ$$

$$-3 \text{ dB} = 20\log_{10}(0.707)$$

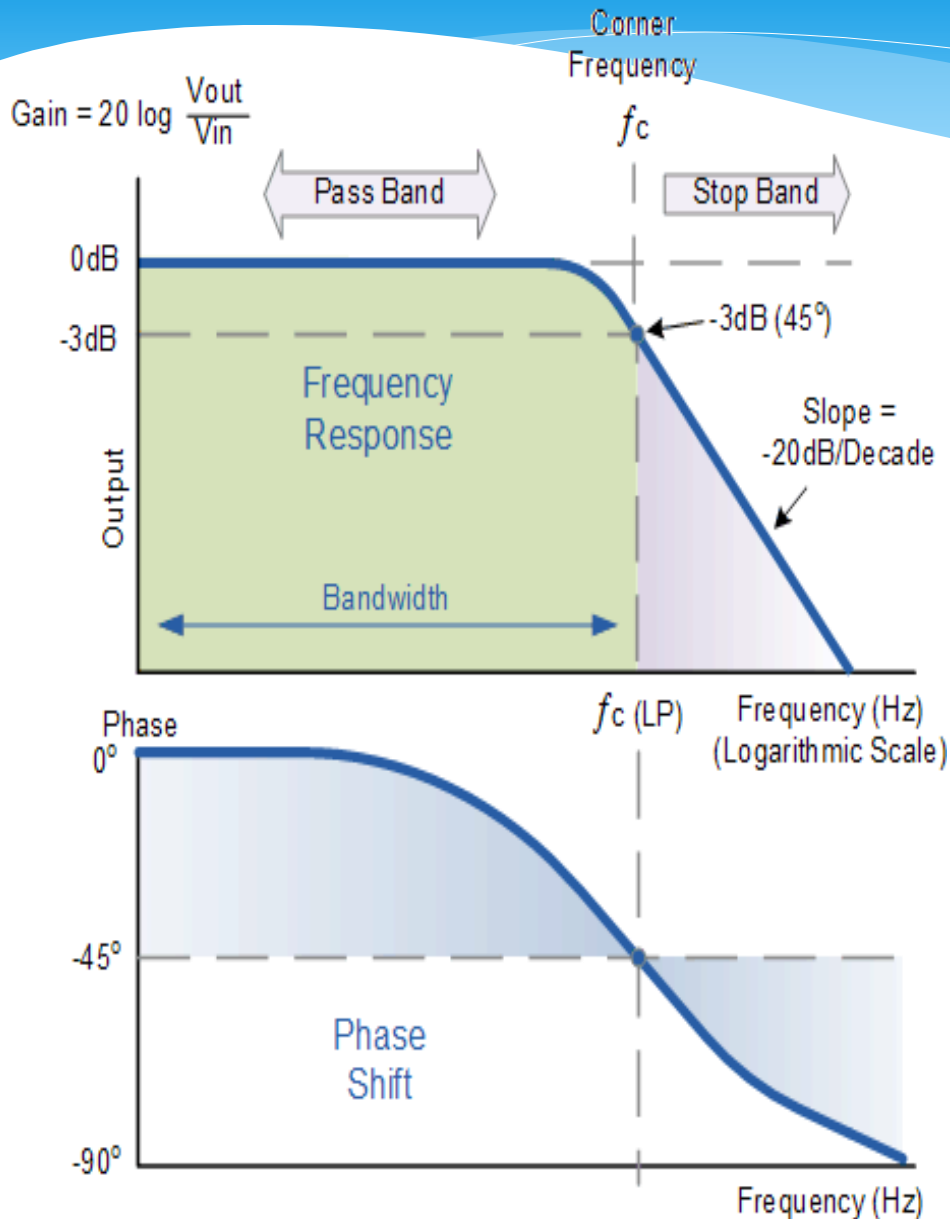

NOTE: we used the modulus of quantities here as we only need the ratio of values to be $(1/\sqrt{2})$, i.e., 0.707. We don't need phases.

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{|X_C|}{\sqrt{R^2 + X_C^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{\frac{1}{\omega C}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

$$\frac{1}{2} = \frac{\left(\frac{1}{\omega C}\right)^2}{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$f_C = \frac{1}{2\pi RC}$$



$$\Rightarrow \omega = \frac{1}{RC}$$

$$\frac{V_o}{V_{in}} = \frac{X_C}{X_C + R} = \frac{1}{1 + R/X_C} = \frac{1}{1 + \frac{R}{1/j\omega C}}$$

$$= \frac{1}{1 - j\omega RC} = \frac{1 + j\omega RC}{1^2 - (j\omega RC)^2} = \frac{1 + j\omega RC}{1 + (\omega RC)^2}$$

$$\frac{V_o}{V_{in}} = \frac{1}{a} + j \frac{\omega RC}{a}$$

$$= x + jy$$

$$\Rightarrow \phi = -\tan^{-1}(y/x)$$

$$\phi = -\tan^{-1}(\omega RC)$$


NOTE: here we didn't use modulus, as we had to consider the phase to find "phi".

Passband of a filter is the range of frequencies that are allowed to pass through the filter with minimum attenuation (usually defined as less than -3 dB of attenuation).

Transition region shows the area where the fall-off occurs.

Stopband is the range of frequencies that have the most attenuation.

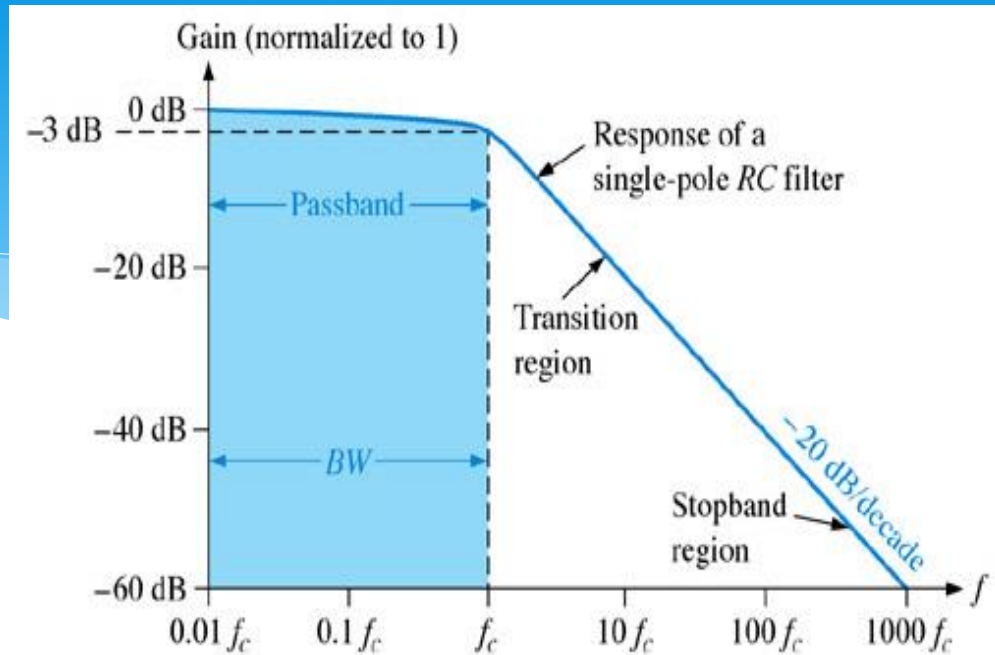
Critical frequency, f_c , (also called the cutoff frequency) defines the end of the passband and normally specified at the point where the response drops - 3 dB (70.7%) from the passband response.



HIGH-PASS FILTER

A high-pass filter allows for easy passage of high-frequency signals from source to load, and difficult passage of low-frequency signals.

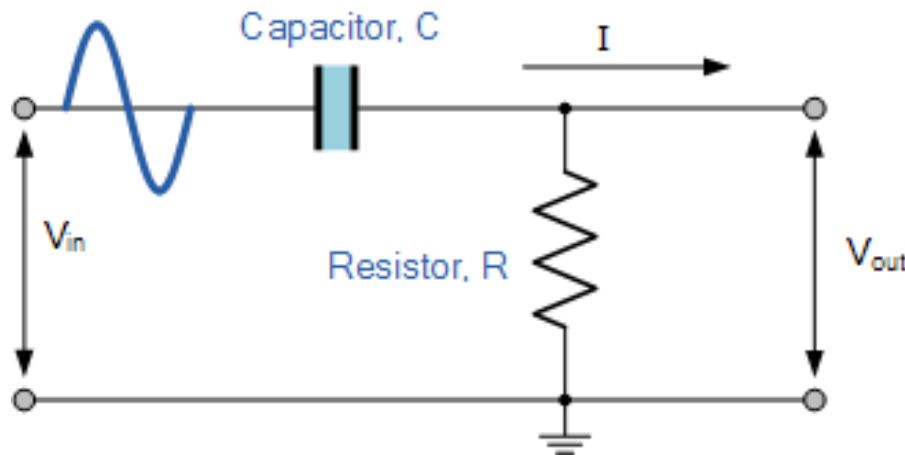
The cutoff frequency for a high-pass filter is that frequency at which the output (load) voltage equals 70.7% of the input (source) voltage. Above the cutoff frequency, the output voltage is greater than 70.7% of the input, and vice versa.



at low f : $X_c \rightarrow \infty$, $V_{out} = 0$
at high f : $X_c \rightarrow 0$, $V_{out} = V_{in}$

First order high pass
filter
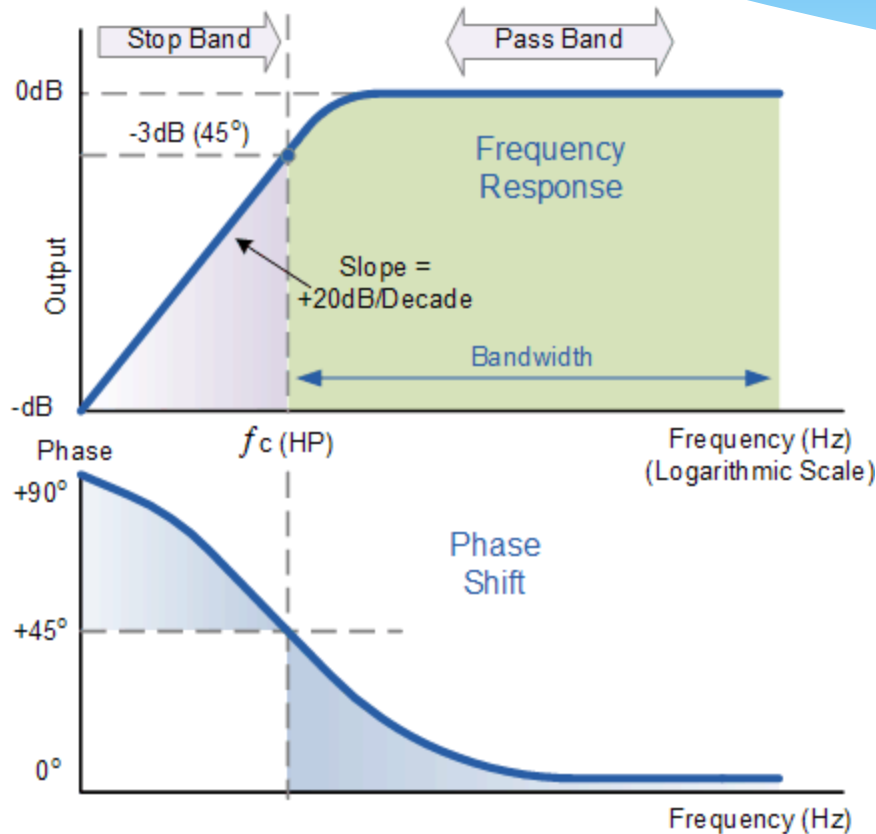
$$\text{Gain (dB)} = 20 \log \frac{V_{\text{out}}}{V_{\text{in}}}$$



$$f_c = \frac{1}{2\pi RC}$$

$$\text{Phase Shift } \phi = \arctan \frac{1}{2\pi fRC}$$


$$\frac{V_o}{V_{in}} = \frac{R}{R + X_c} \rightarrow$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + \frac{1}{j\omega RC}}$$

$$\rightarrow \phi = -\tan^{-1}(-1/\omega RC)$$

BAND-PASS FILTER

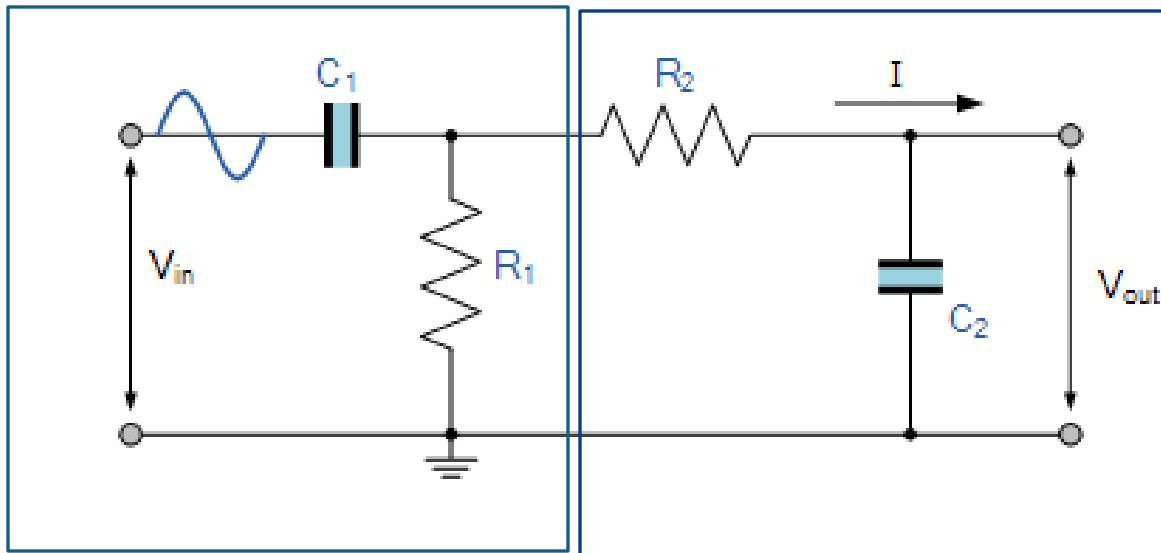
- By connecting or “cascading” together a single Low Pass Filter circuit with a High Pass Filter circuit, we can produce another type of passive RC filter that passes a selected range or “band” of frequencies that can be either narrow or wide while attenuating all those outside of this range.
- known commonly as a Band Pass Filter



To set the first band pass frequency f_1 .
Freq of high pass part

To set the second band pass frequency f_2 . Freq of low pass part

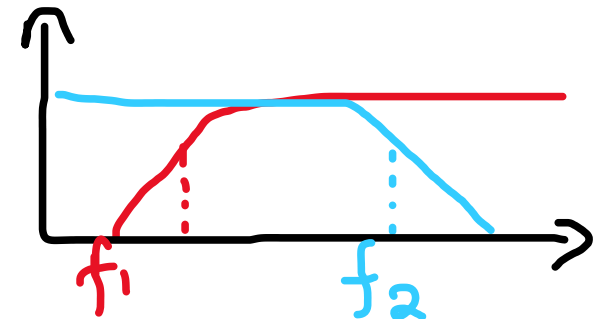Cutoff Frequency of high pass filter must be less than that of low pass filter for the cascading to be a band pass filter




Some definition

- * The bandwidth (BW) is defined as the difference between the upper critical frequency and the lower critical frequency.

$$\text{Bandwidth} = F_h - F_l$$

- * The frequency about which the pass band is centered is called the center frequency, f_0 and defined as the geometric mean of the critical frequencies.
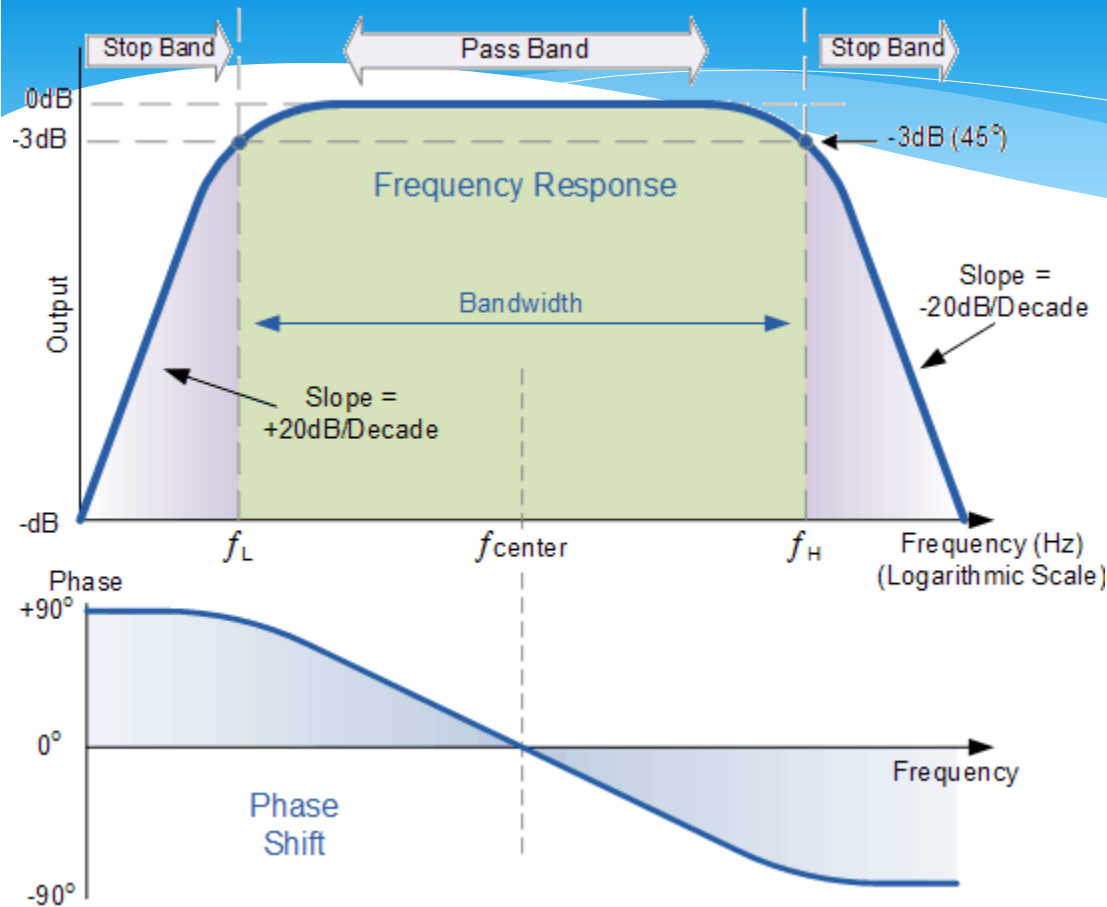
$$\text{Centre frequency} = \sqrt{F_l * F_h}$$



$$\text{Bandwidth} = F_h - F_l$$

$$\text{Centre frequency} = \sqrt{F_l * F_h}$$

Find separately F_h and F_l by using the respective formulae of cutoff freq.

$$f_l = f_1 = \frac{1}{2\pi R_1 C_1}$$

$$f_h = f_2 = \frac{1}{2\pi R_2 C_2}$$

F_l and F_h are lower cutoff and higher cutoff frequencies of the filter respectively.

And f_1 and f_2 (they are the freq of high pass and low pass filter respectively)


So we have:

Lower cutoff = F_l = freq. of high pass filter = f_1

And F_h = freq. Of low pass filter = f_2

BAND-STOP FILTER

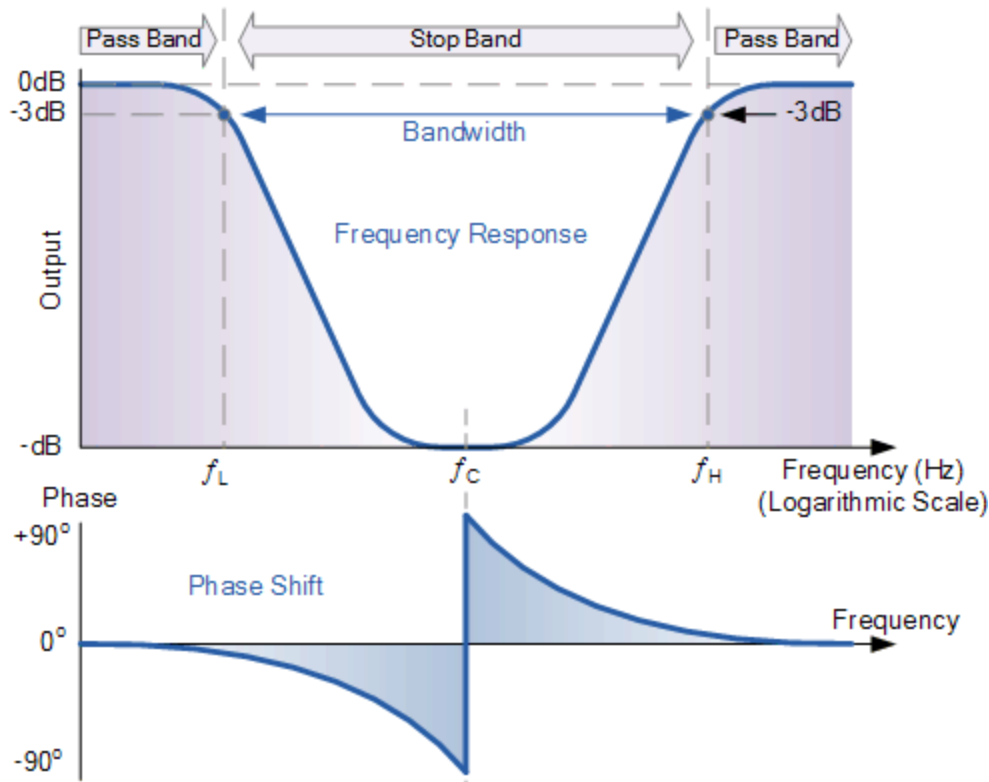- combine the low and high pass filter to produce another kind of RC filter network
- that can block or at least severely attenuate a band of frequencies within these two cut-off frequency points.



Opposite to Band-pass filter:


Cutoff Frequency of high pass filter must be greater than that of low pass filter for the cascading to be a band-stop filter

- Band-pass filters are constructed by combining a low pass filter in series with a high pass filter
- Band stop filters are created by combining together the low pass and high pass filter sections in a “parallel” type configuration as shown.

Cutoff
frequency is
200Hz




Cutoff
frequency is
800Hz

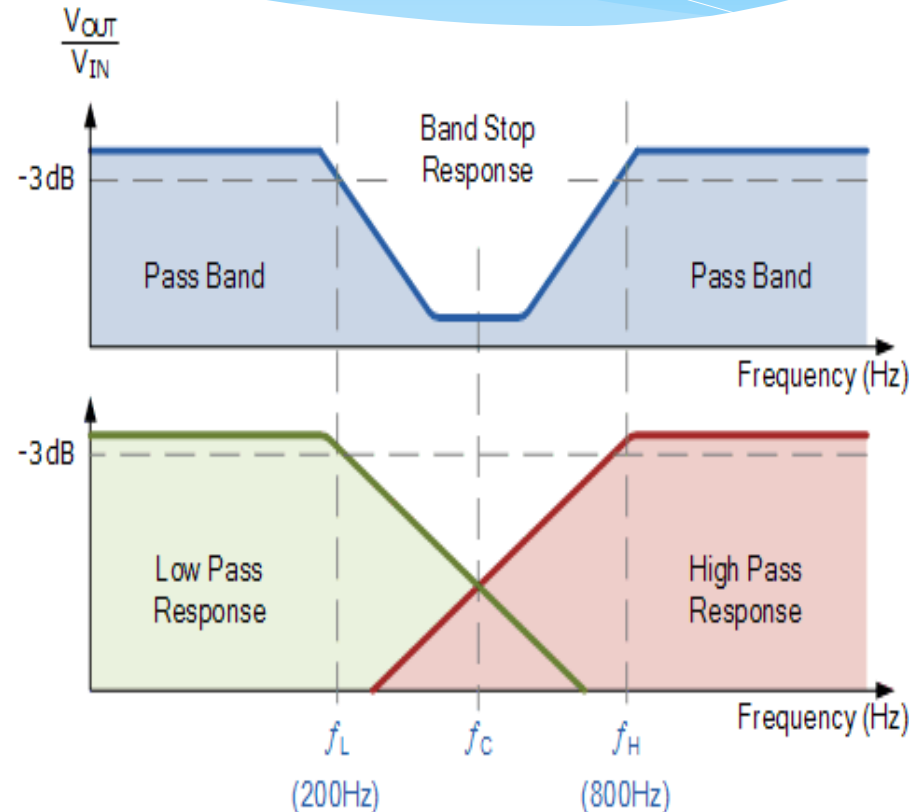

CASCADING

eg →


Second order Low Pass Filter

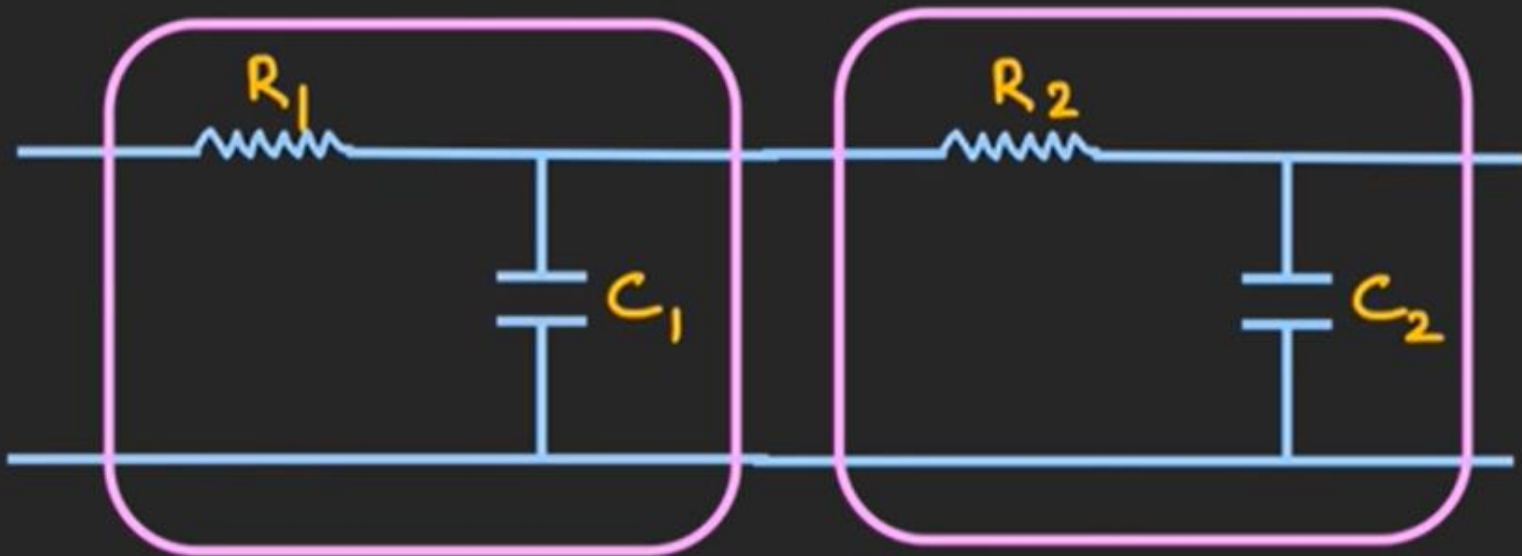

$$f_c = \frac{1}{2\pi \times \sqrt{R_1 C_1 R_2 C_2}}$$

* Roll-off rate increases * Cutoff frequency decreases.

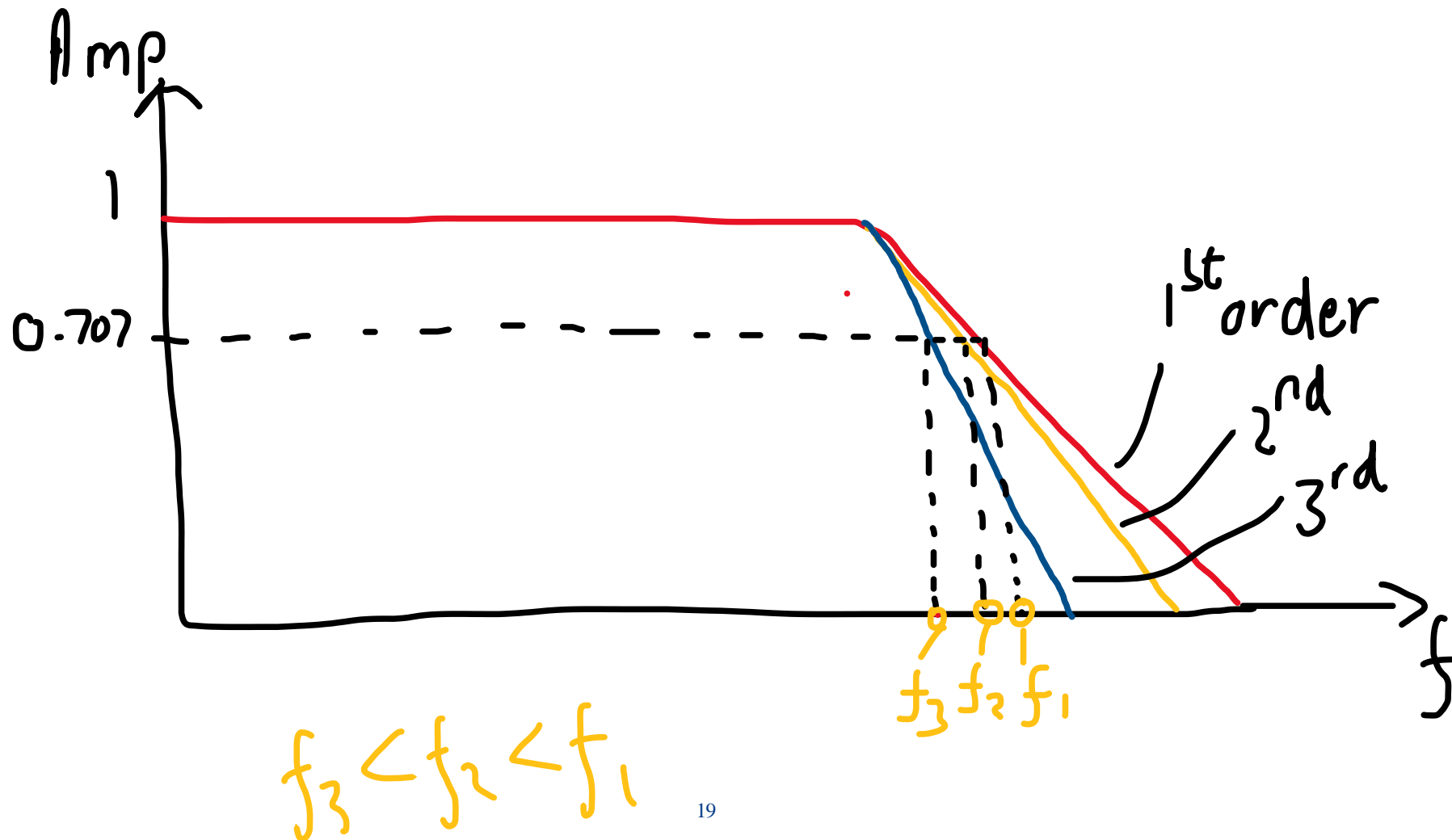Example- consider General low pass response





Active Filter

Introduction

- Filters are circuits that are capable of *passing signals within a band* of frequencies while *rejecting or blocking* signals of frequencies *outside this band*. This property of filters is also called “frequency selectivity”.
- Filter can be passive or active filter.

Passive filters: The circuits built using RC, RL, or RLC circuits.

Active filters : The circuits that employ one or more op-amps in the design an addition to resistors and capacitors

Advantages of Active Filters over Passive Filters

- Active filters can be designed to provide required gain, and hence no attenuation as in the case of passive filters
- No loading problem, because of high input resistance and low output resistance of op-amp it isolates the load from input.
- Active Filters are cost effective as a wide variety of economical op-amps are available.



-> LOADING PROBLEM: While calculating V_{o1} we assume open circuit at output, for this assumption to be right any external load applied must be $\gg R_1$ (like here $R_2 \geq 10 \cdot R_1$ must hold). If this is not true filter response is not as expected (cutoff freq changes).

-> Occurs while cascading or when an external load comparable to R_1 is connected at o/p.

Applications

- Active filters are mainly used in communication and signal processing circuits.
- They are also employed in a wide range of applications such as entertainment, medical electronics, etc.

Active Filters


➤ There are 4 basic categories of active filters:

- 1. Low-pass filters**
- 2. High-pass filters**
- 3. Band-pass filters**
- 4. Band-reject filters**


➤ Each of these filters can be built by using op-amp as the active element combined with RC, RL or RLC circuit as the passive elements.

- The **bandwidth** of an **ideal** low-pass filter is equal to f_c :


$$BW = f_c$$

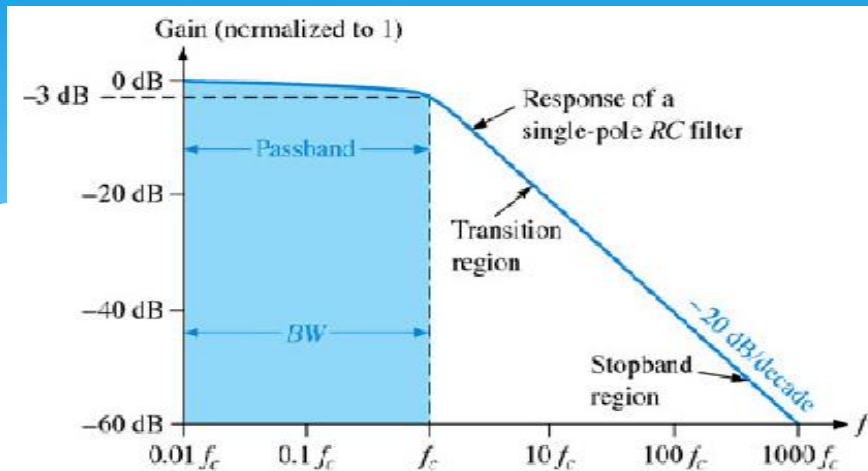

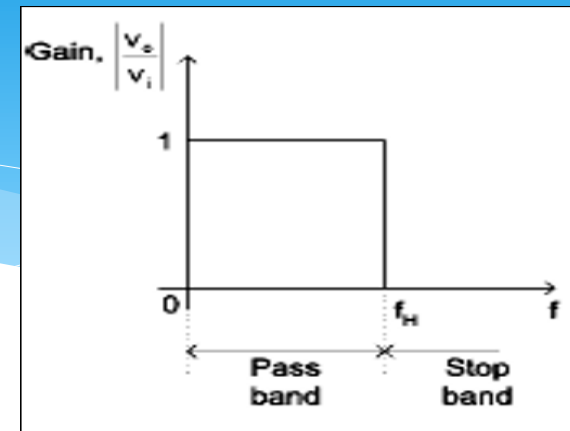
(a) Comparison of an ideal low-pass filter response with actual response



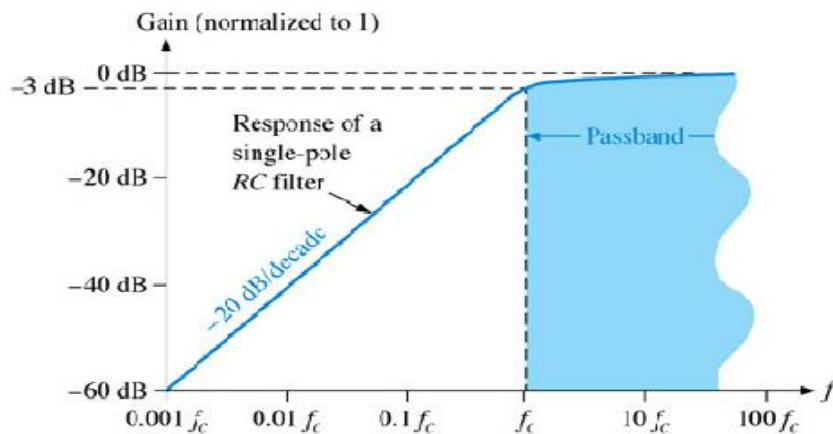- The passband of a high-pass filter is all frequencies above the critical frequency.



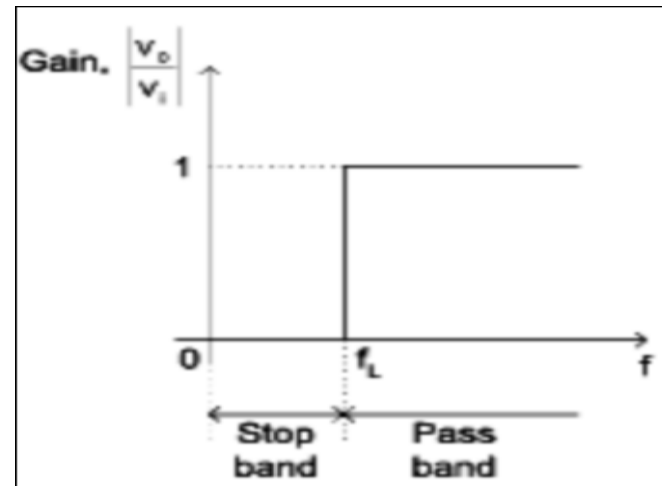(a) Comparison of an ideal high-pass filter response with actual response




➤ The **bandwidth (BW)** for a band-pass filter is defined as the **difference** between the **upper critical frequency (f_{c2})** and the **lower critical frequency (f_{c1})**.

$$BW = f_{c2} - f_{c1}$$

➤ The frequency about which the pass band is centered is called the **center frequency, f_o** and defined as the geometric mean of the critical frequencies.

$$f_o = \sqrt{f_{c1} f_{c2}}$$

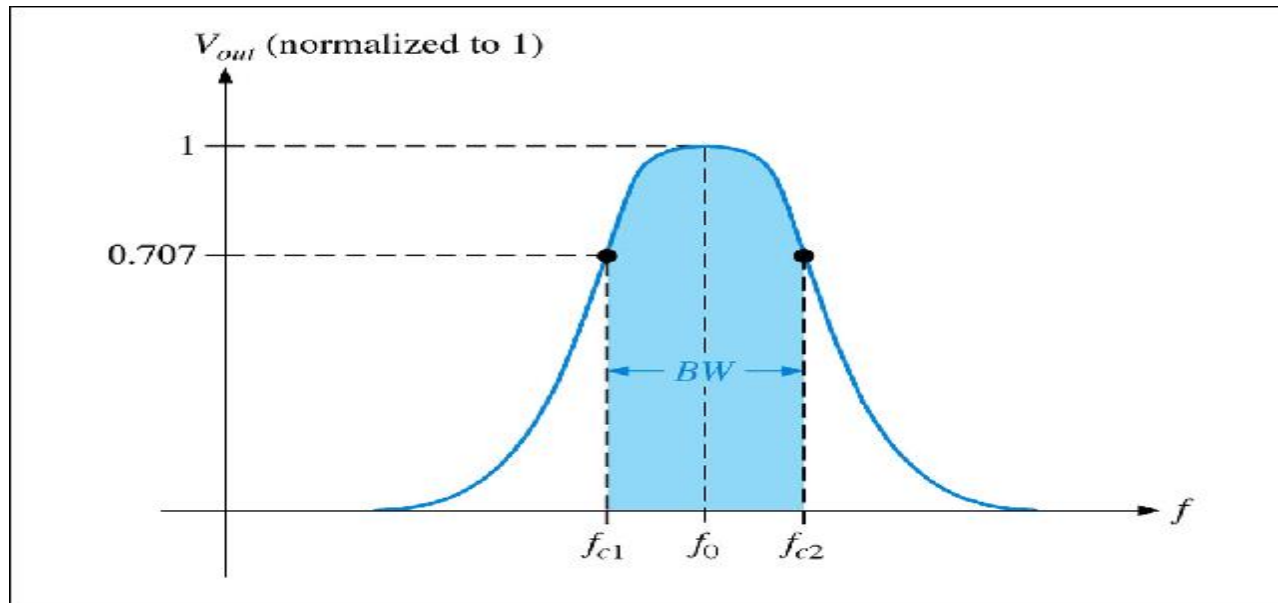

➤ The **quality factor (Q)** of a band-pass filter is the ratio of the center frequency to the bandwidth.

$$Q = \frac{f_o}{BW}$$

➤ The higher value of Q , the narrower the bandwidth and the better the selectivity for a given value of f_o .

➤ ($Q > 10$) as a narrow-band or ($Q < 10$) as a wide-band

➤ The quality factor (Q) can also be expressed in terms of the damping factor (DF) of the filter as :

$$Q = \frac{1}{DF}$$

FILTER RESPONSE CHARACTERISTICS

➤ There are **3 most common** characteristics of filter response :


- i) **Butterworth** characteristic
- ii) **Chebyshev** characteristic
- iii) **Bessel** characteristic.

➤ Each of the characteristics is identified by the **shape of the response curve**.

➤ Also known as

"Filter approximations"

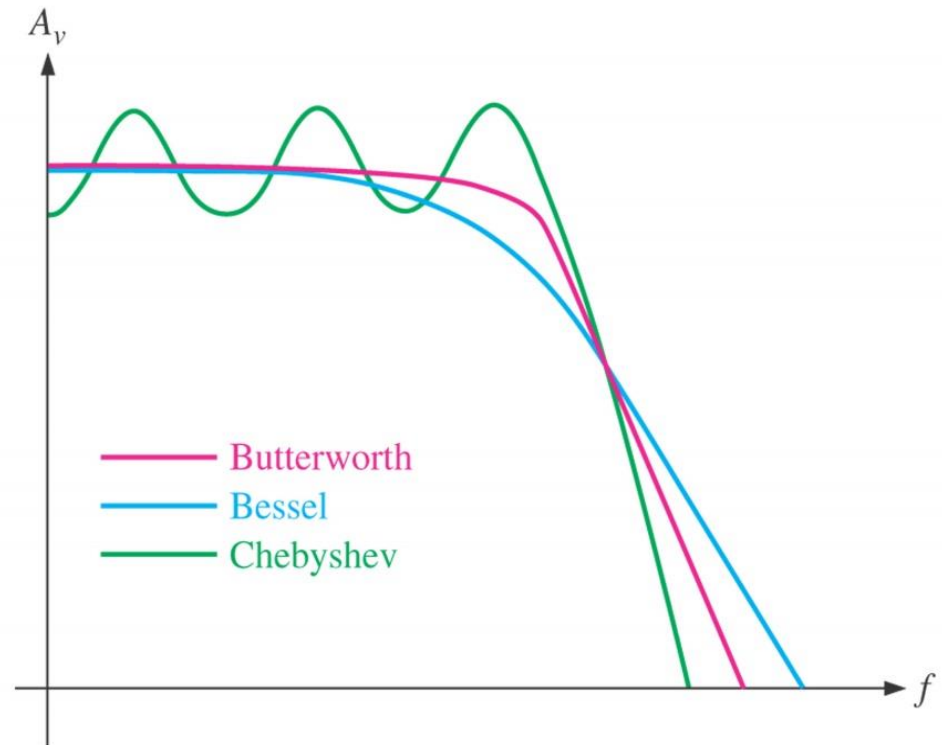
➤ Others are: **Inverse Chebyshev** and **Elliptical**



Comparative plots of three types of filter response characteristics.


Butterworth Characteristic

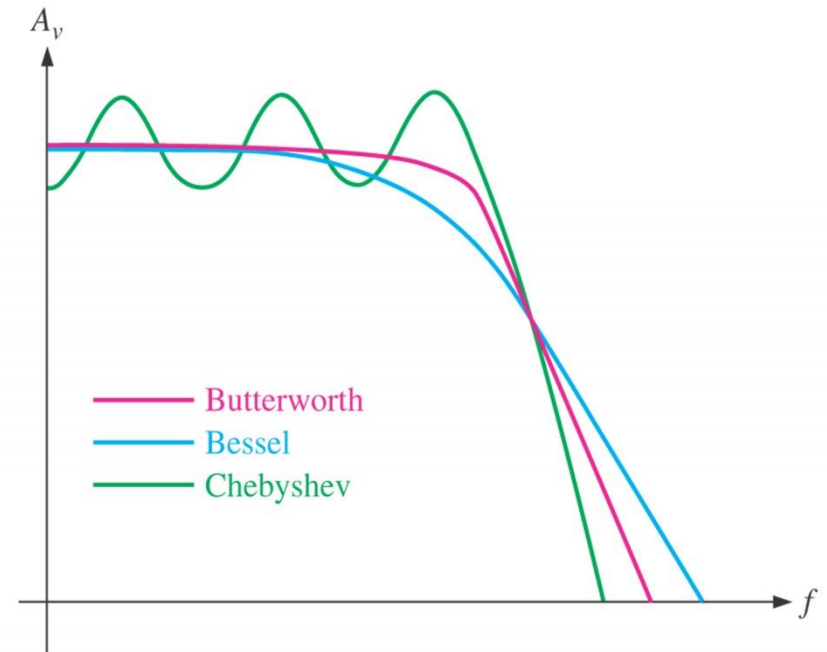- Filter response is characterized by **flat amplitude response** in the passband.
- Provides a roll-off rate of -20 dB/decade/pole.
- Filters with the Butterworth response are normally used when all frequencies in the passband must have the **same gain**.




Chebyshev Characteristic

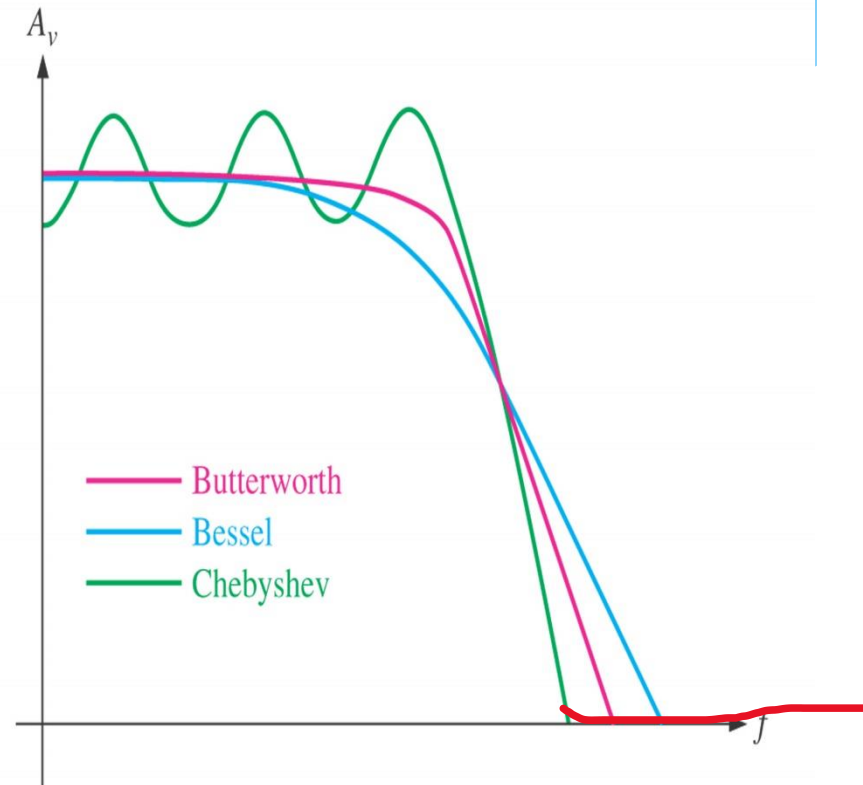- Filter response is characterized by **overshoot** or **ripples** in the passband.
- Provides a roll-off rate greater than -20 dB/decade/pole.
- Filters with the Chebyshev response can be implemented with **fewer poles** and **less complex circuitry** for a given roll-off rate




Bessel Characteristic

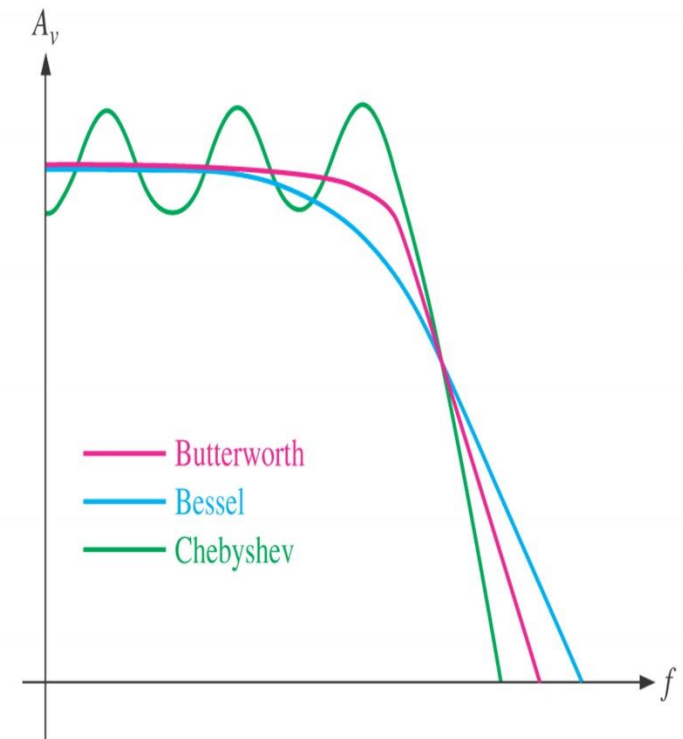- Filter response is characterized by a **linear characteristic**, meaning that the phase shift increases linearly with frequency.
- Filters with the Bessel response are used for filtering pulse waveforms without distorting the shape of waveform.



THE TRANSFER FUNCTION IS THE FILTER

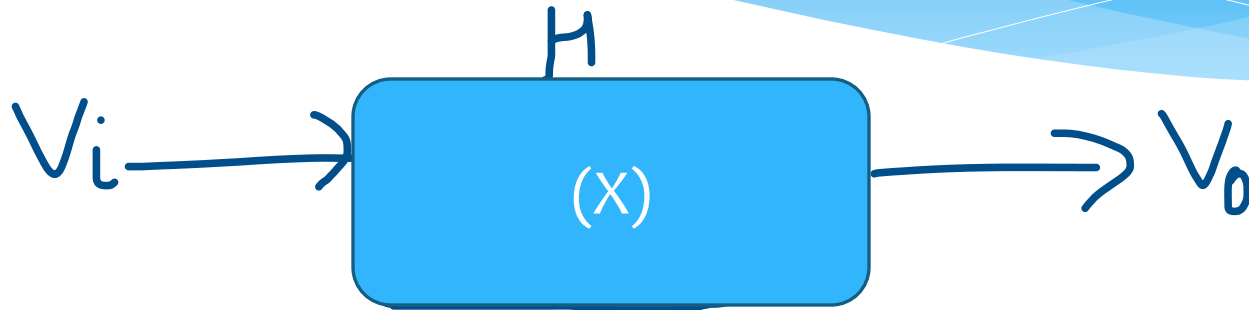

$$\text{Let } H() = \frac{V_o()}{V_i()} = \frac{X_c}{R + X_c}$$

* System order is always equal to number of poles of the transfer function.

So the order of filter is equal to the no. of poles the filter has

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1/c s}{R + 1/c s} = \frac{1}{1 + RCs} \quad \left. \vphantom{\frac{1}{1 + RCs}} \right\} \begin{array}{l} \text{has 1 pole} \\ \text{at } s = -\frac{1}{RC} \end{array}$$


So only by knowing the transfer function you can get a good idea about the filter.

-> if you have the transfer function you can factorise the denominator and get the no. of poles and thus you get info about the order of filter.

-> also no. of reactive elements = no. of poles

→ apply on reduced ckt
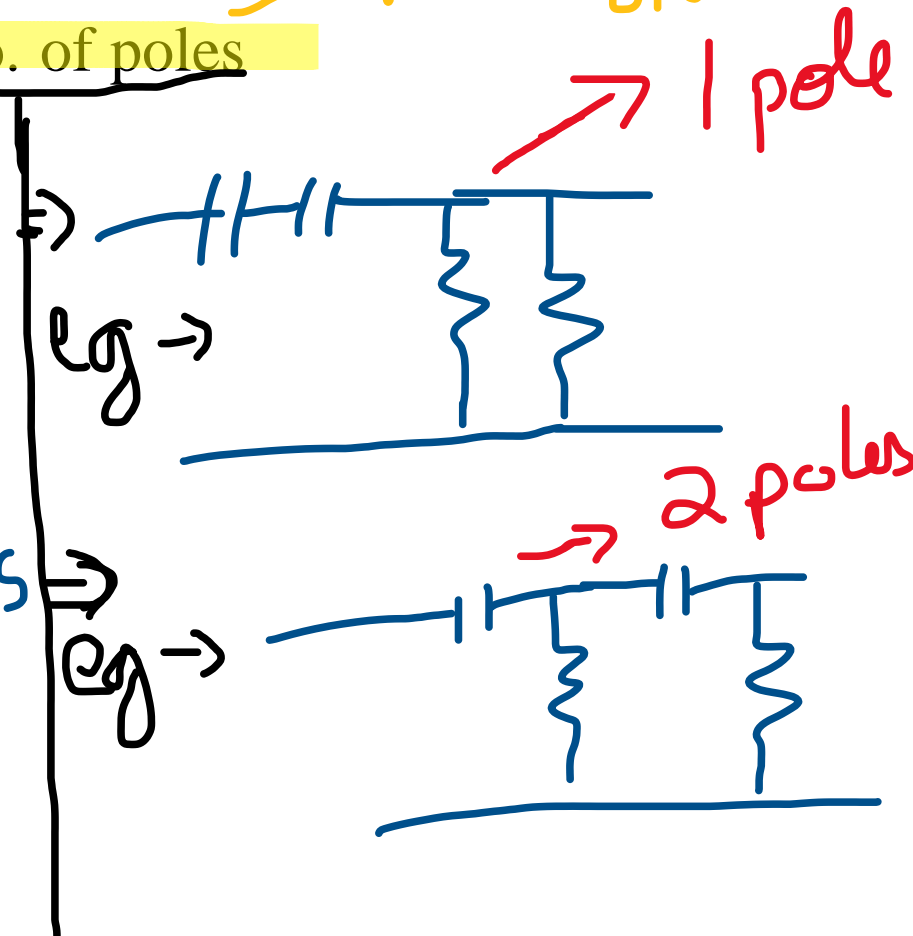
$$\begin{array}{l} \swarrow \searrow \\ X_C = \frac{1}{C\omega} \quad X_L = \omega L \\ X_C(s) = \frac{1}{Cs} \quad X_L(s) = Ls \end{array}$$




DAMPING FACTOR

➤ The **damping factor (DF)** of an active filter determines which response characteristic the filter exhibits.

- This active filter consists of **an amplifier, a negative feedback circuit** and **RC circuit**.
- The amplifier and feedback are connected in a **non-inverting configuration**.

➤ DF is determined by the negative feedback and defined as :

$$DF = 2 - \frac{R_1}{R_2}$$

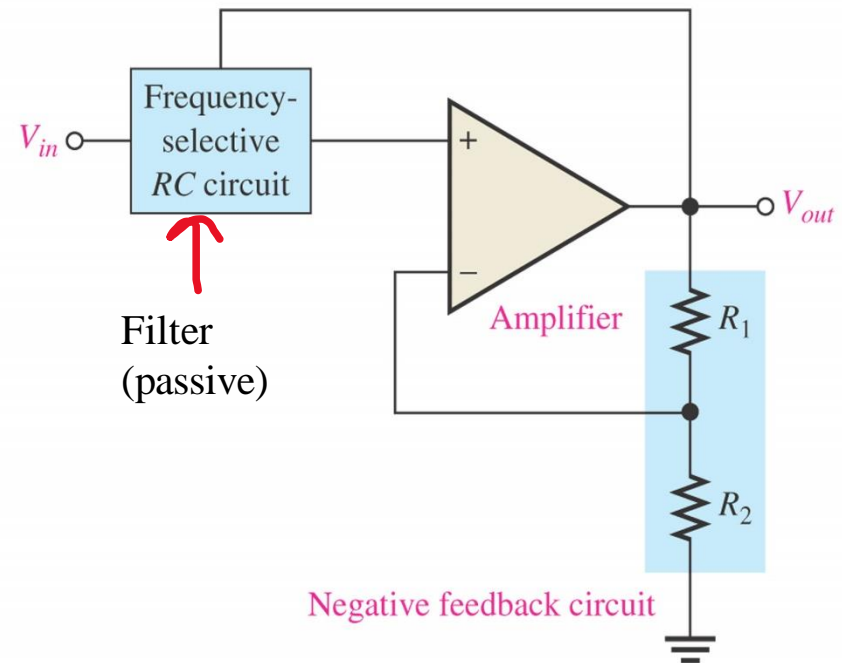


General diagram of active filter

SOME POINTS TO REMEMBER:

- The value of DF required to produce a desired response characteristics depends on **order** (number of poles) of the filter.
- A pole (single pole) is simply **one resistor** and **one capacitor**.
- The **more poles** filter has, the faster its roll-off rate

Revision negative feedback:

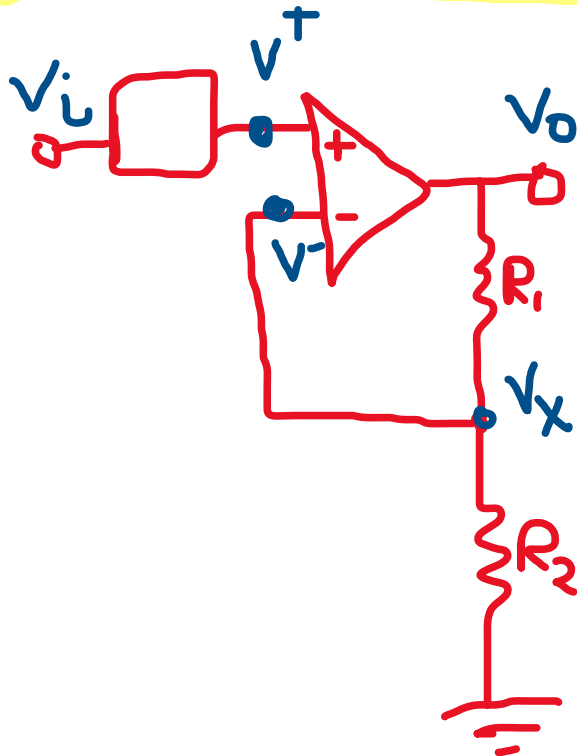


$$V_o = A(V^+ - V^-) \quad \Bigg| \quad V^- = V_x = \frac{V_o R_2}{R_1 + R_2}$$

as $V_o \uparrow \Rightarrow V_x$
 due to $V^+ \uparrow$ or $V^- \downarrow$

$\Rightarrow V^-$
 \Downarrow
 $(V^+ - V^-)$
 \Downarrow
 V_o

CRITICAL FREQUENCY AND ROLL-OFF RATE

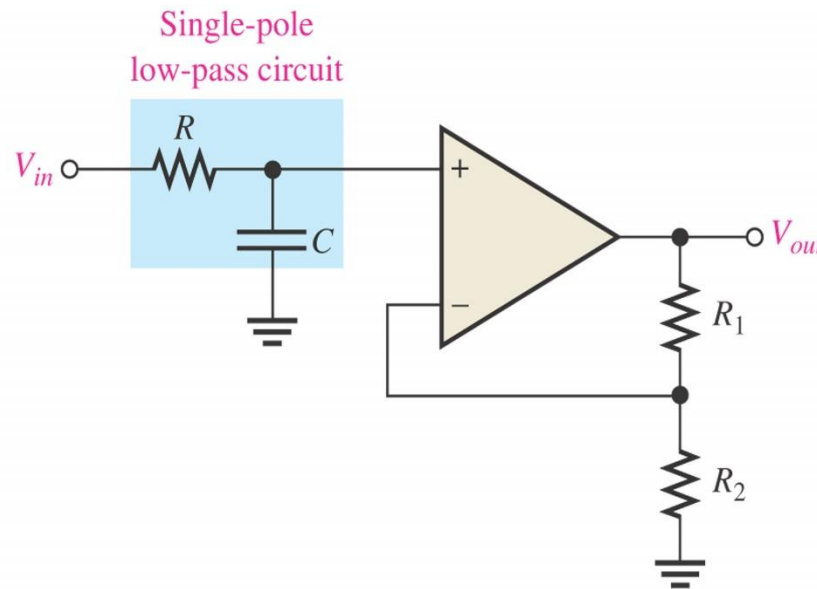

One-pole (first-order) low-pass filter.

- The **critical frequency, f_c** is determined by the values of **R** and **C** in the frequency-selective RC circuit.
- Each **RC** set of filter components represents a **pole**.
- **Greater roll-off rates** can be achieved with **more poles**.
- Each pole represents a **-20dB/decade** increase in roll-off.

- For a single-pole (first-order) filter, the critical frequency is :



$$f_c = \frac{1}{2\pi RC}$$

- The above formula can be used for both low-pass and high-pass filters.


➤ The number of poles determines the roll-off rate of the filter. For example, a Butterworth response produces -20dB/decade/pole.

This means that:

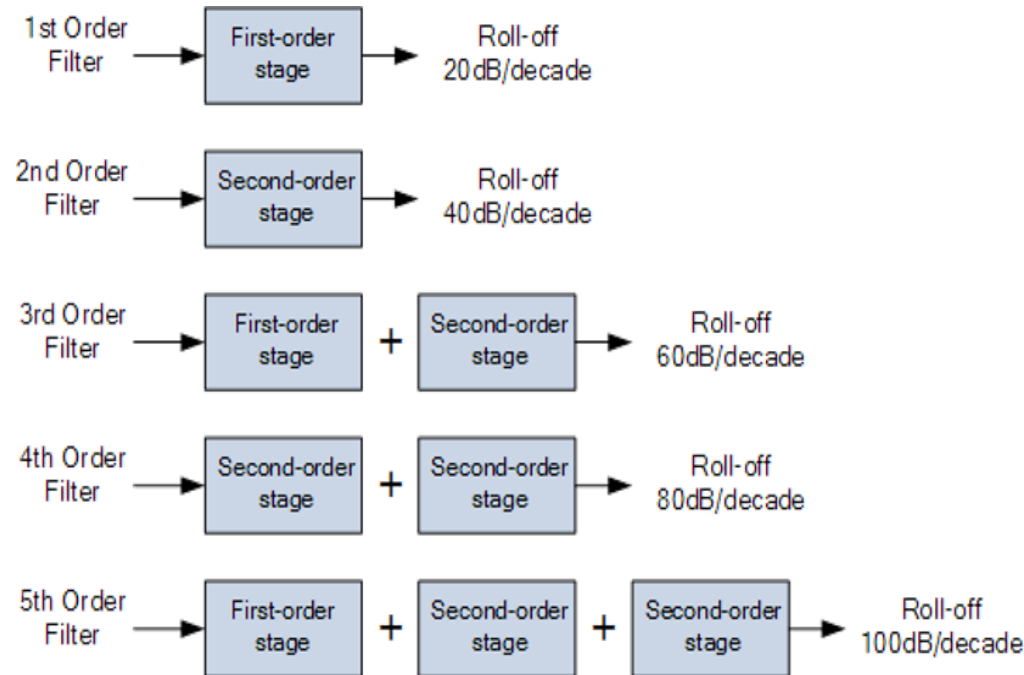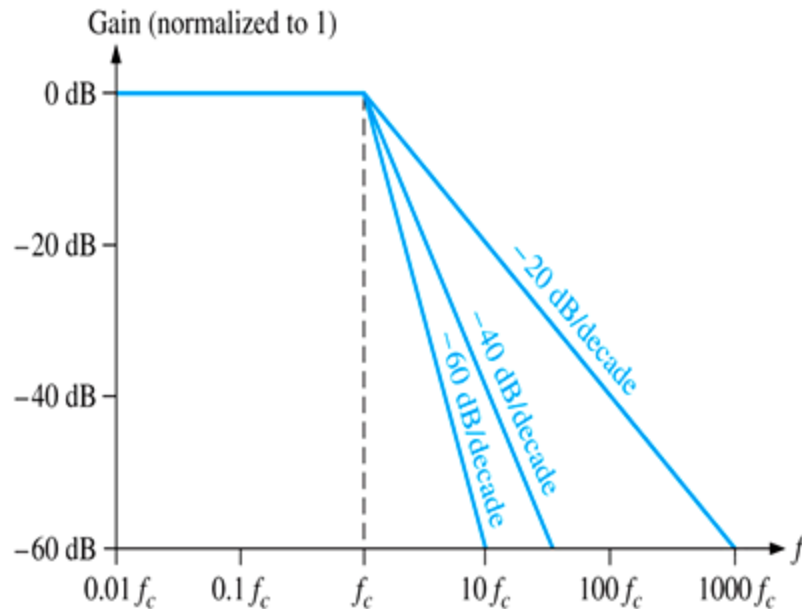- **One-pole (first-order)** filter has a roll-off of -20 dB/decade
- **Two-pole (second-order)** filter has a roll-off of -40 dB/decade
- **Three-pole (third-order)** filter has a roll-off of -60 dB/decade



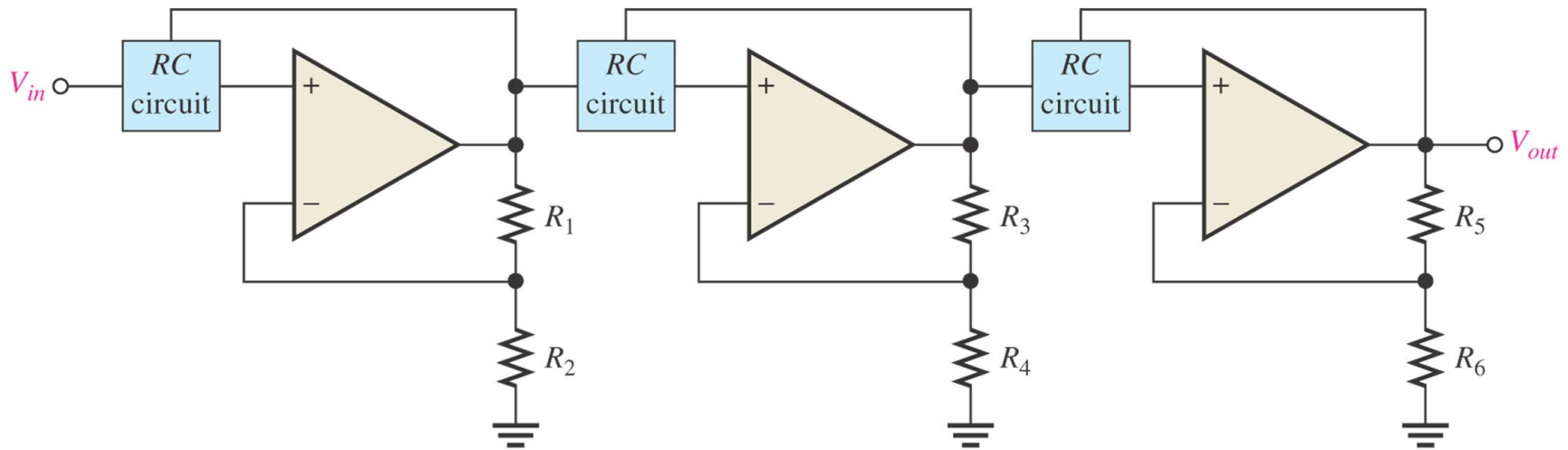➤ The number of filter poles can be increased by *cascading*. To obtain a filter with three poles, you can cascade 3 single-pole filters (as shown below), but more preferred way is to cascade a two-pole with one-pole filters (we will see this in later slides)




Three-pole (third-order) low-pass filter.

ACTIVE LOW-PASS FILTERS

Advantages of active filters over passive filters (R, L, and C elements only):

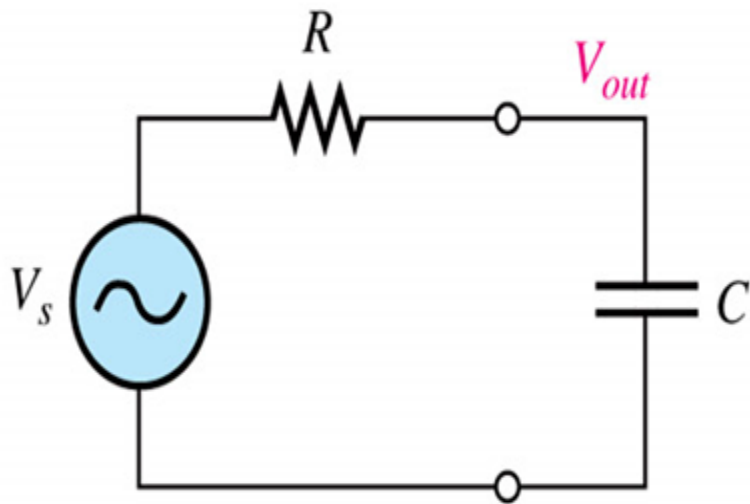1. By containing the op-amp, active filters can be designed to provide required gain, and hence **no signal attenuation** as the signal passes through the filter.
2. **No loading problem**, due to the high input impedance of the op-amp prevents excessive loading of the driving source, and the low output impedance of the op-amp prevents the filter from being affected by the load that it is driving.
3. **Easy to adjust over a wide frequency range** without altering the desired response.

➤ Figure below shows the basic Low-Pass filter circuit



(b) Basic low-pass circuit

At critical frequency,

Resistance = Capacitance

$$R = X_c$$



$$R = \frac{1}{\omega_c C}$$

$$R = \frac{1}{2\pi f_c C}$$

So, critical frequency ;

$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

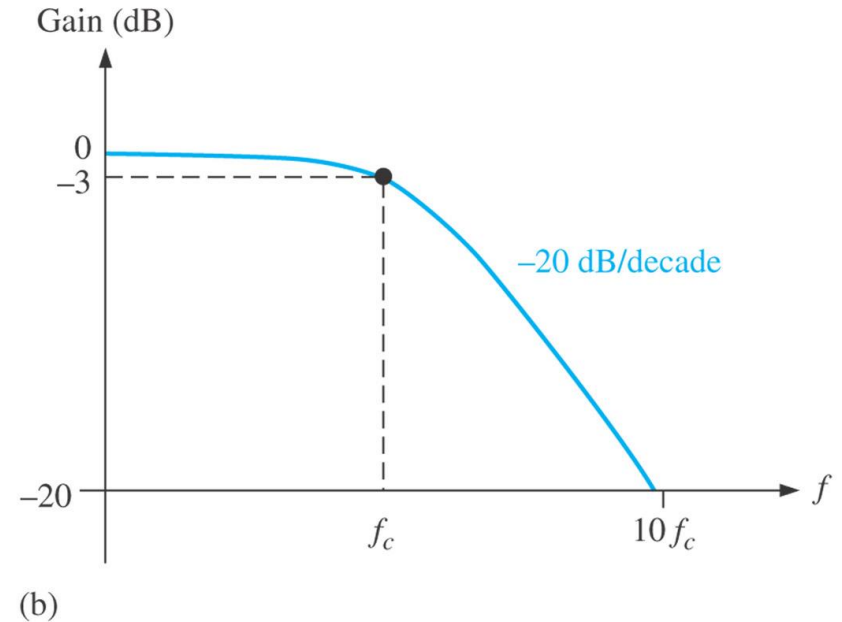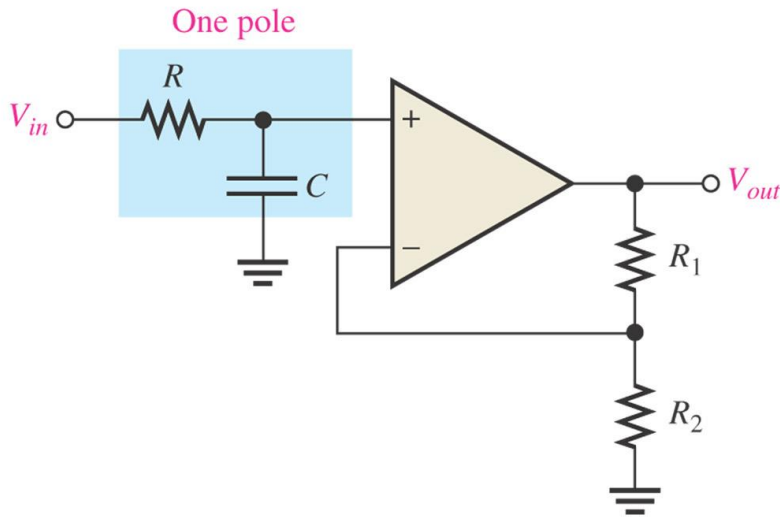

Single-pole active low-pass filter and response curve.

➤ This filter provides a roll-off rate of -20 dB/decade above the critical frequency.

- The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


Closed loop gain in non-inverting configuration

$A_{cl(NI)}$

$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$


- The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

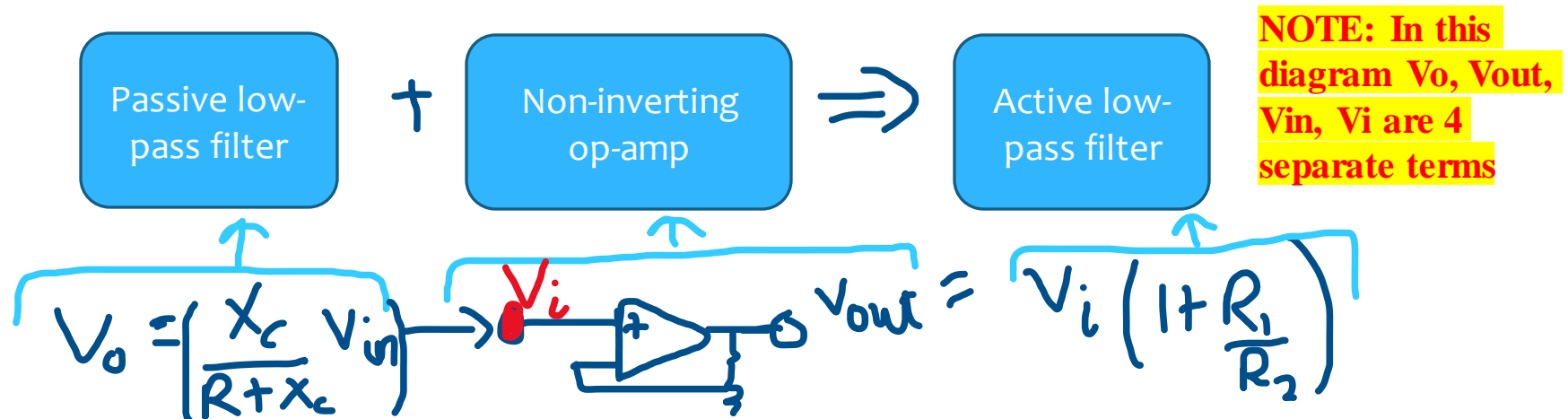

Sallen-Key Low-Pass Filter

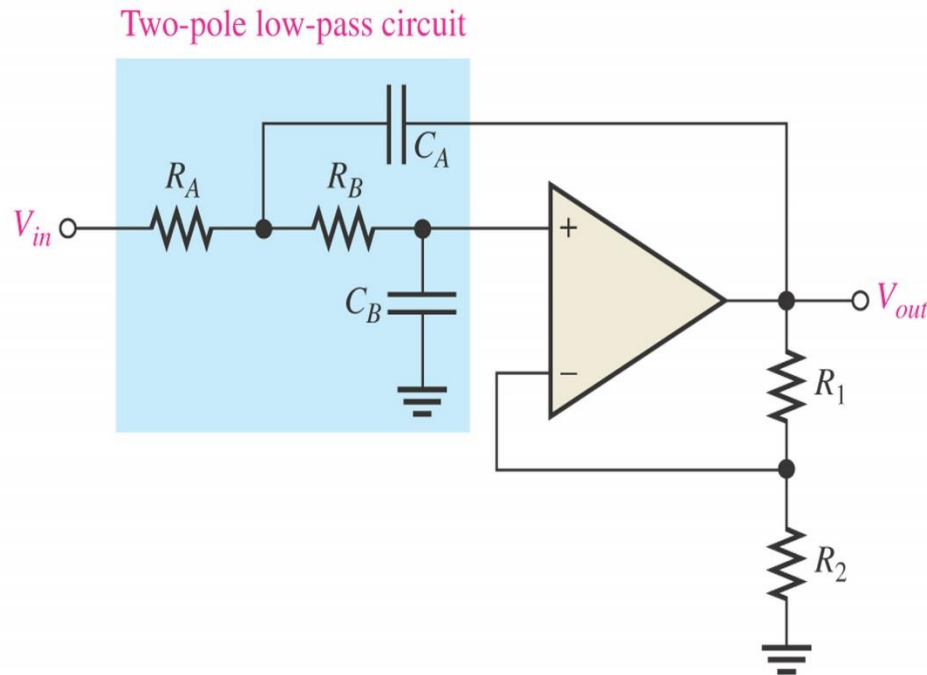- **Sallen-Key** is one of the most common configurations for a **second order** (two-pole) filter.



- There are two low-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c** (assuming a Butterworth characteristics).
- One RC circuit consists of **R_A** and **C_A** , and the second circuit consists of **R_B** and **C_B** .

Basic Sallen-Key low-pass filter.

➤ The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

➤ For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$

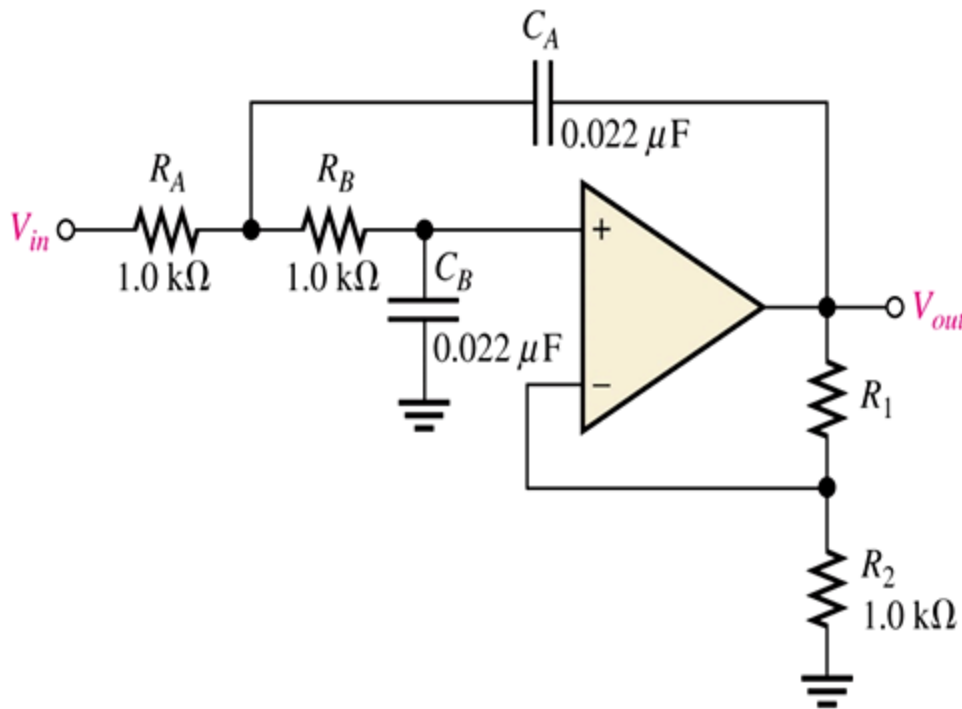Example :

- Determine critical frequency
- Set the value of R_1 for Butterworth response. Given that Butterworth response for second order is 0.586



- Critical frequency


- Butterworth response

Butterworth \Rightarrow flat amplitude response
 \Rightarrow Same gain

And, Here we have gain = $1 + (R_1/R_2)$
 \Rightarrow throughout response is same = R_1/R_2


Cascading Low-Pass Filter

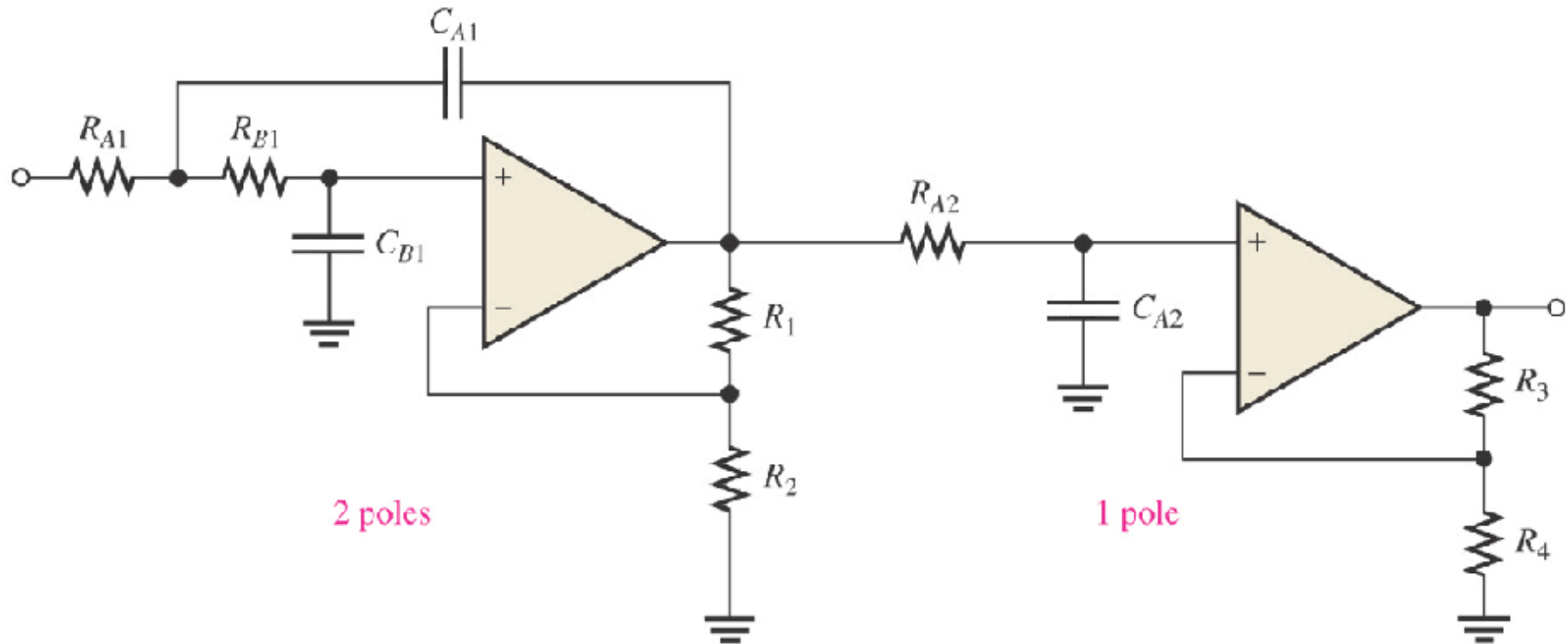- A three-pole filter is required to provide a roll-off rate of **-60 dB/decade**. This is done by cascading a **two-pole Sallen-Key low-pass filter** and a **single-pole low-pass filter**.



Cascaded low-pass filter: third-order configuration.

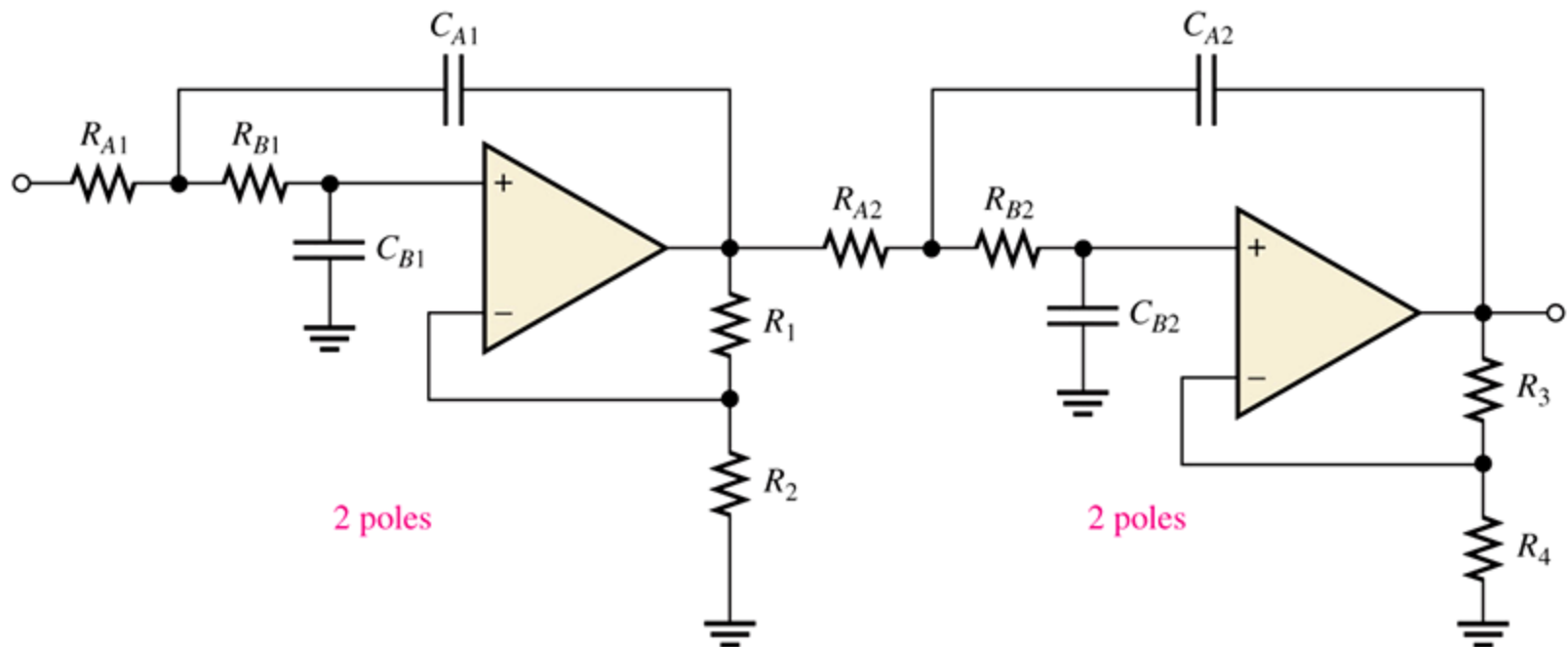➤ A **four-pole filter** is required to provide a roll-off rate of **-80 dB/decade**. This is done by cascading a **two-pole Sallen-Key low-pass filter** and a **two-pole Sallen-Key low-pass filter**.




(b) Fourth-order configuration

Cascaded low-pass filter: fourth-order configuration.

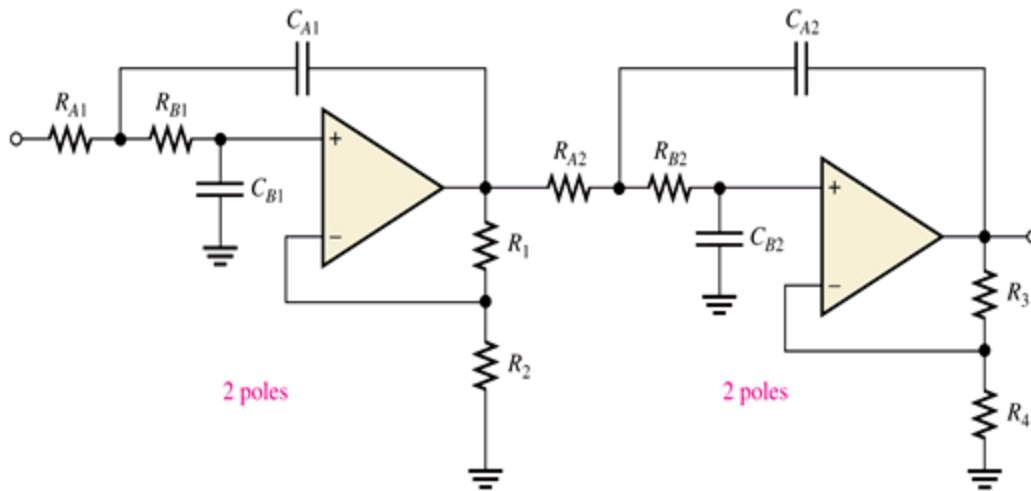Example :

- Determine the capacitance values required to produce a critical frequency of 2680 Hz if all resistors in RC low pass circuit is 1.8kΩ



(b) Fourth-order configuration

$$f_c = \frac{1}{2\pi RC}$$


$$C = \frac{1}{2\pi f_c R} = 0.033 \mu F$$

$$C_{A1} = C_{B1} = C_{A2} = C_{B2} = 0.033 \mu f$$

- Both stages must have the same f_c . Assume equal-value of capacitor

ACTIVE HIGH-PASS FILTERS

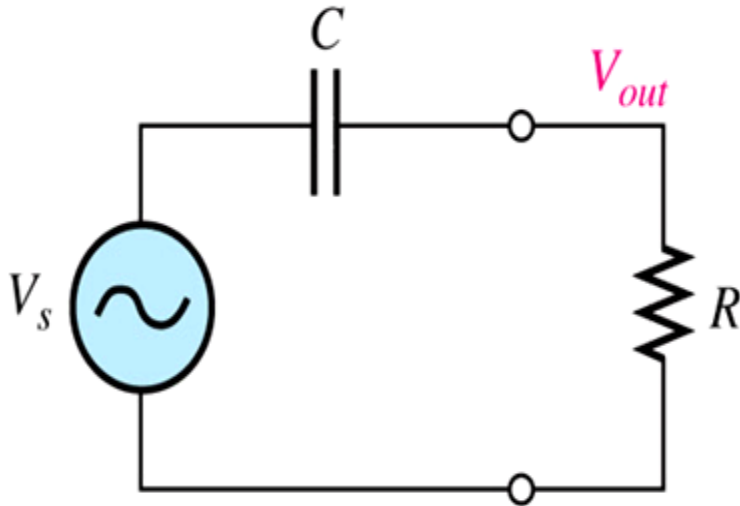- Figure below shows the basic High-Pass filter circuit :



(b) Basic high-pass circuit

At critical frequency,

Resistance = Capacitance

$$R = X_c$$

$$R = \frac{1}{\omega_c C}$$


$$R = \frac{1}{2\pi f_c C}$$

So, critical frequency ;


$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

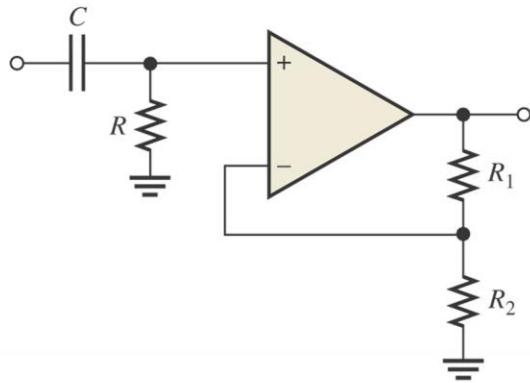- In high-pass filters, the roles of the **capacitor** and **resistor** are **reversed** in the RC circuits as shown from Figure (a). The negative feedback circuit is the same as for the low-pass filters.
- Figure (b) shows a high-pass active filter with a -20dB/decade roll-off



(a)

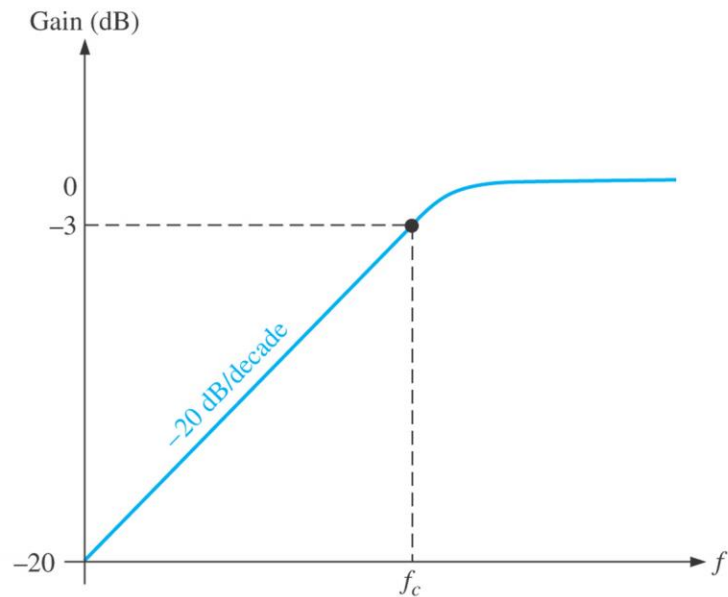

(b)

Single-pole active high-pass filter and response curve.

- The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

- The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

Sallen-Key High-Pass Filter

- Components R_A , C_A , R_B , and C_B form the **second order** (two-pole) frequency-selective circuit.
- The position of the resistors and capacitors in the frequency-selective circuit are **opposite** in low pass configuration.
- There are two high-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c**
- The **response characteristics** can be optimized by proper selection of the **feedback resistors**, R_1 and R_2 .

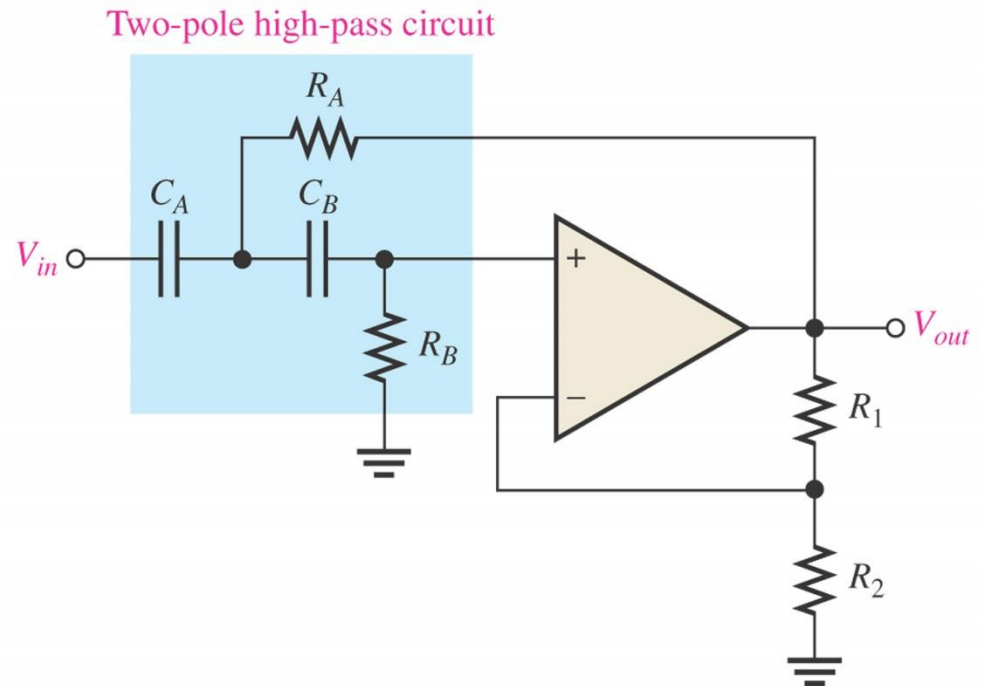

Basic Sallen-Key high-pass filter.

- The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

- For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$

Cascading High-Pass Filter

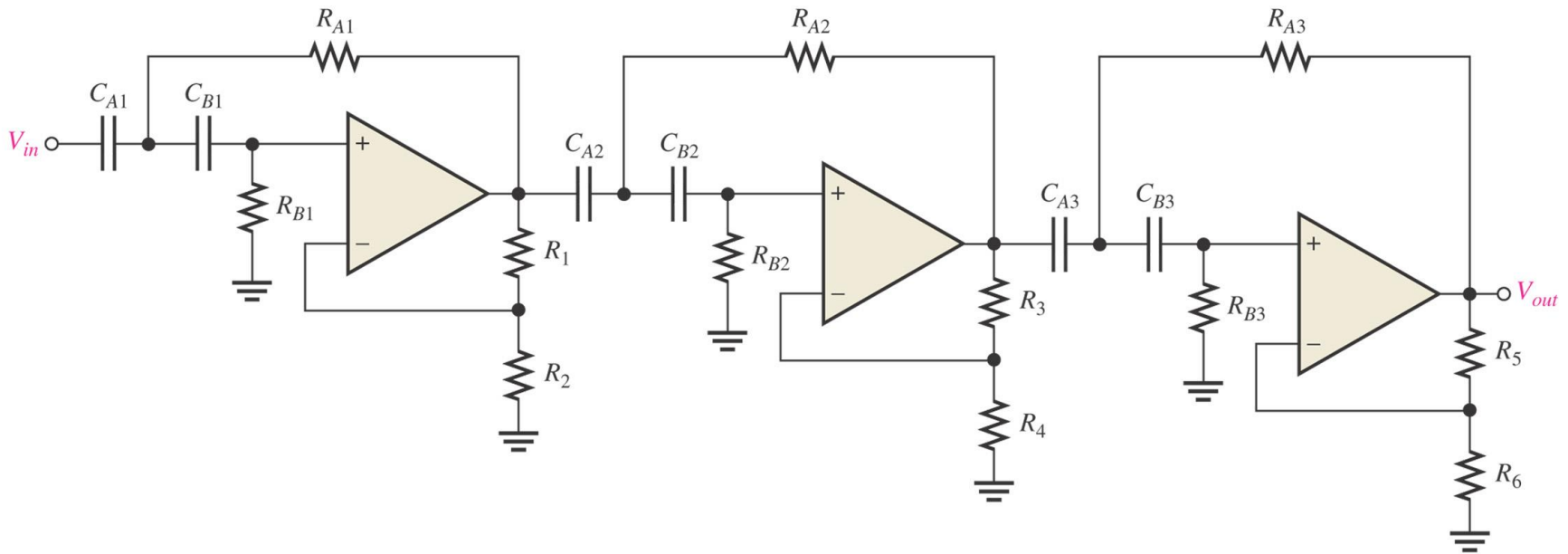
- As with the low-pass filter, first- and second-order high-pass filters can be cascaded to provide three or more poles and thereby create faster roll-off rates.
- A **six-pole high-pass filter** consisting of **three Sallen-Key two-pole** stages with the roll-off rate of **-120 dB/decade**.




Sixth-order high-pass filter

ACTIVE BAND-PASS FILTERS


Cascaded Low-Pass and High-Pass Filters

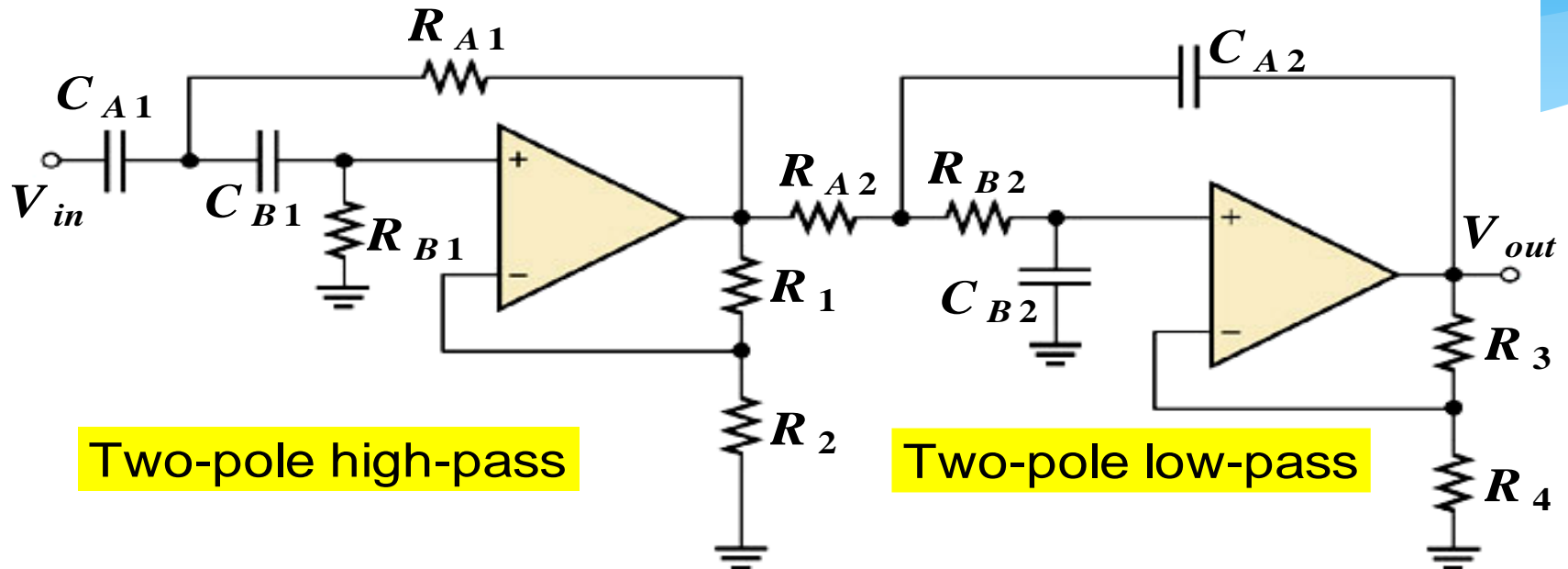

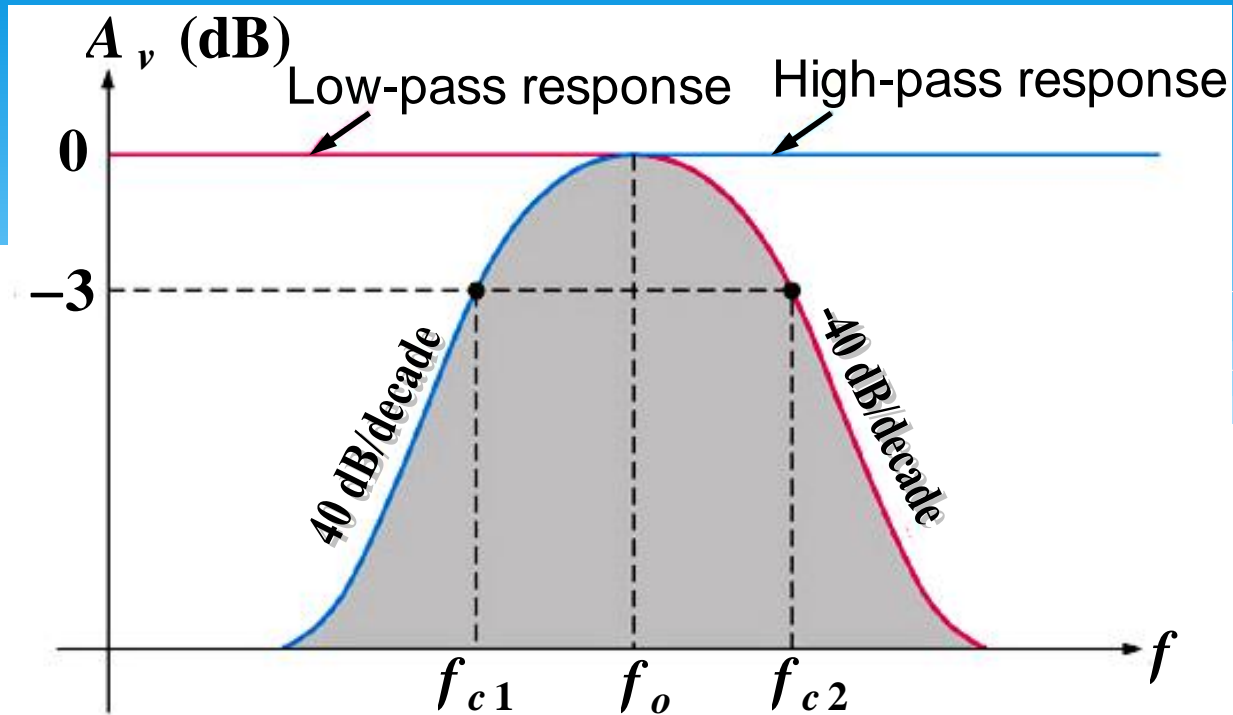- Band-pass filter is formed by cascading a two-pole high-pass and two pole low-pass filter.
- Each of the filters shown is Sallen-Key Butterworth configuration, so that the roll-off rate are -40dB/decade.



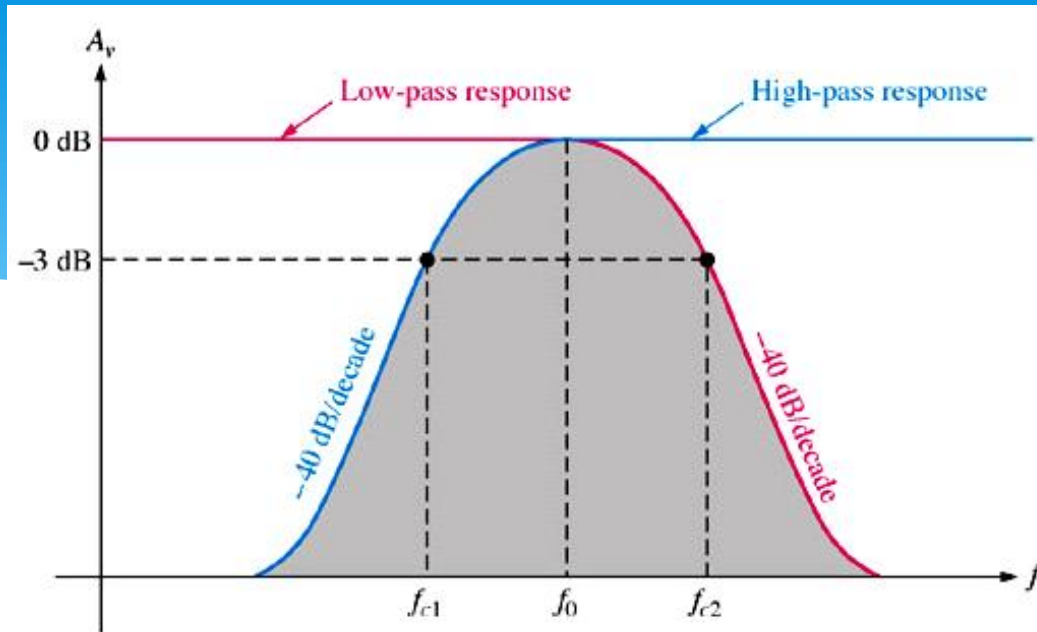- The lower frequency f_{c1} of the passband is the critical frequency of the high-pass filter.
- The upper frequency f_{c2} of the passband is the critical frequency of the low-pass filter.



➤ The following formulas express the three frequencies of the band-pass filter.

$$f_{c1} = \frac{1}{2\pi\sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$


$$f_{c2} = \frac{1}{2\pi\sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

➤ If equal-value components are used in implementing each filter,

$$f_c = \frac{1}{2\pi RC}$$

Multiple-Feedback Band-Pass Filter

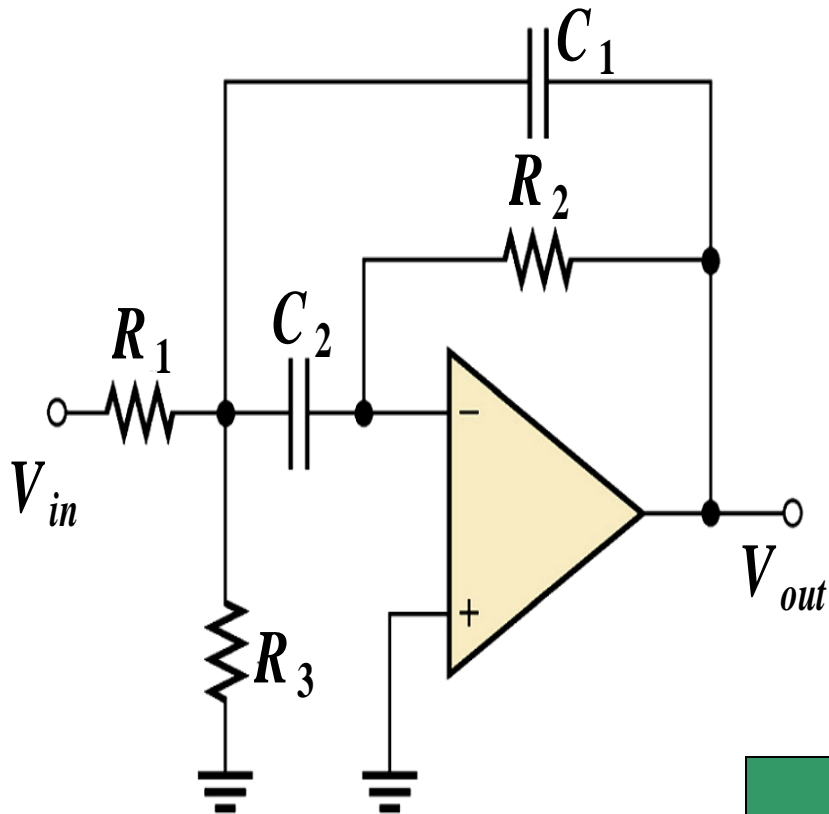

- The low-pass circuit consists of R_1 and C_1 .
- The high-pass circuit consists of R_2 and C_2 .
- The feedback paths are through C_1 and R_2 .
- Center frequency;

$$f_0 = \frac{1}{2\pi\sqrt{(R_1 // R_3)R_2C_1C_2}}$$

- By making $C_1 = C_2 = C$, yields

$$f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$$

- The resistor values can be found by using following formula

$$R_1 = \frac{Q}{2\pi f_o C A_o}$$

$$R_2 = \frac{Q}{\pi f_o C}$$



$$R_3 = \frac{Q}{2\pi f_o C (2Q^2 - A_o)}$$

- The maximum gain, A_o occurs at the center frequency.

$$A_o = \frac{R_2}{2R_1}$$

ACTIVE BAND-STOP FILTERS

Multiple-Feedback Band-Stop Filter

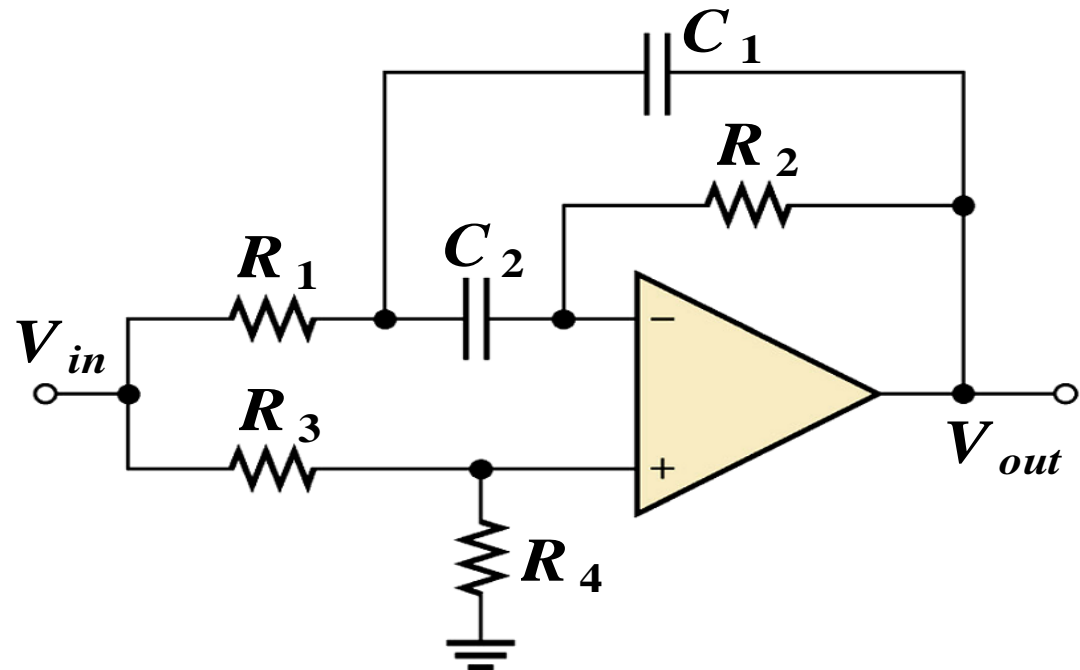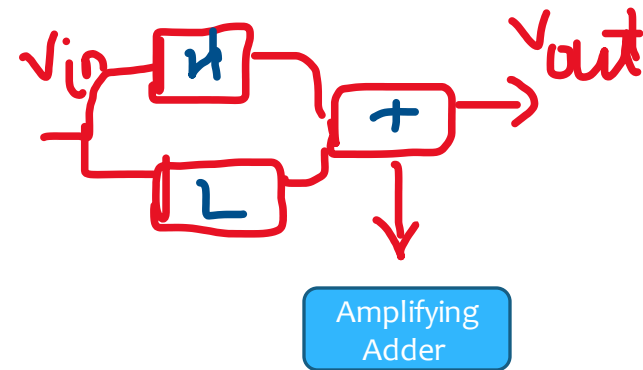

- The configuration is similar to the band-pass version BUT R_3 has been moved and R_4 has been added.
- The BSF is opposite of BPF in that it blocks a specific band of frequencies

FILTER RESPONSE MEASUREMENT

- Measuring frequency response can be performed with typical bench-type equipment.
- It is a process of setting and measuring frequencies both outside and inside the known cutoff points in predetermined steps.
- Use the output measurements to plot a graph.
- More accurate measurements can be performed with sweep generators along with an oscilloscope, a spectrum analyzer, or a scalar analyzer.

SUMMARY

- The bandwidth of a low-pass filter is the same as the upper critical frequency.
- The bandwidth of a high-pass filter extends from the lower critical frequency up to the inherent limits of the circuit.
- The band-pass passes frequencies between the lower critical frequency and the upper critical frequency.

- A band-stop filter rejects frequencies within the upper critical frequency and upper critical frequency.
- The Butterworth filter response is very flat and has a roll-off rate of -20 B
- The Chebyshev filter response has ripples and overshoot in the passband but can have roll-off rates greater than -20 dB

- The Bessel response exhibits a linear phase characteristic, and filters with the Bessel response are better for filtering pulse waveforms.
- A filter pole consists of one RC circuit. Each pole doubles the roll-off rate.
The Q of a filter indicates a band-pass filter's selectivity. The higher the Q the narrower the bandwidth.
- The damping factor determines the filter response characteristic.