




# CONTINUUM

WORKSHOP-2

Introduction to OpAmps
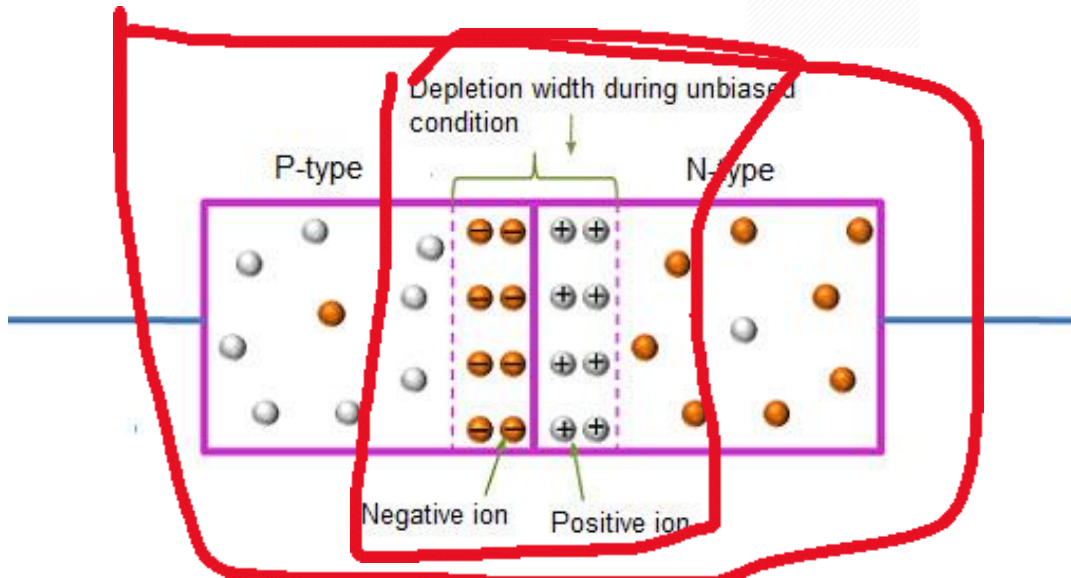
# WHAT IS DIODE?



Electronic devices created by bringing together a  $p$ -type and  $n$ -type region within the same semiconductor lattice. Used for rectifiers, LED etc. It is represented by symbol



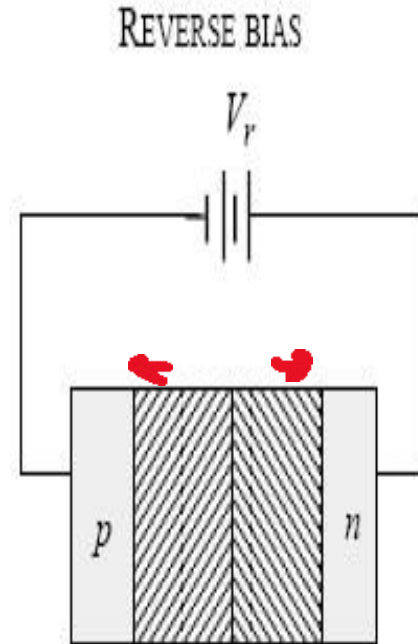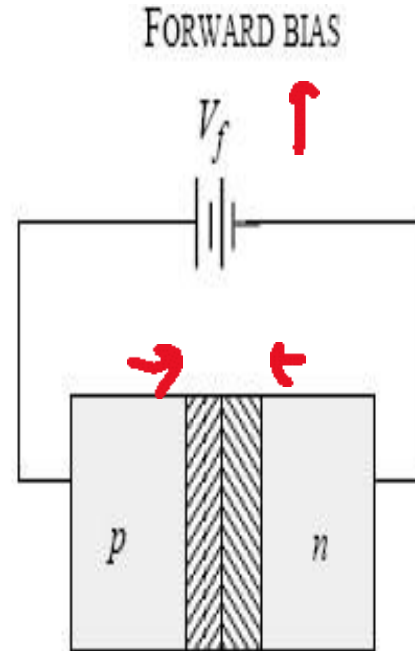
# Biasing of Diode

Forward Bias : Connect positive of the Diode to positive **of** supply...negative of Diode to negative of supply

Reverse Bias: **Connect** positive of the Diode to negative of supply...negative of diode to positive of supply.



# I-V characteristics of Ideal diode

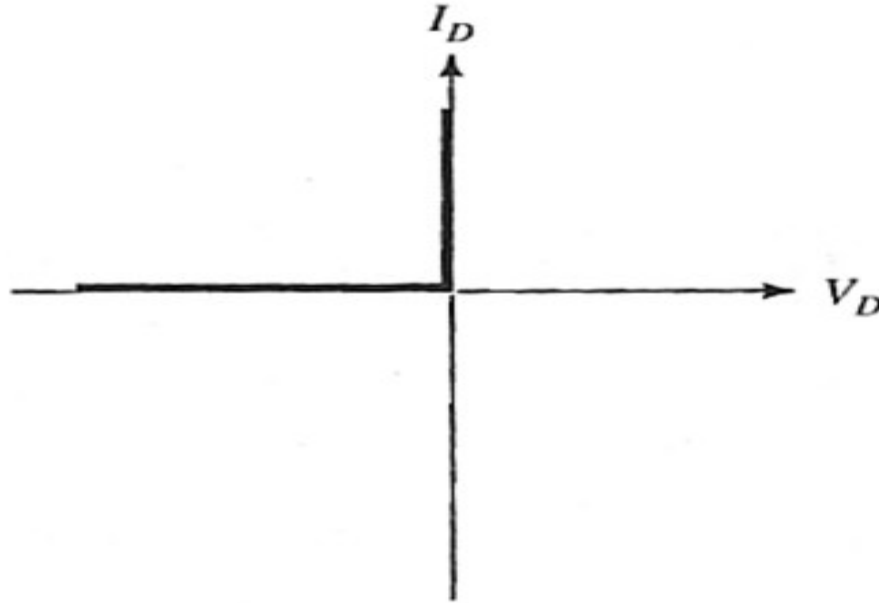

# Characteristics of Ideal Diode

» Conducts in one direction.




» Conduct current when “Forward Biased” ( Zero resistance/Short circuit)



» Do not conduct when “Reverse Biased”  
(Infinite resistance/Open circuit)



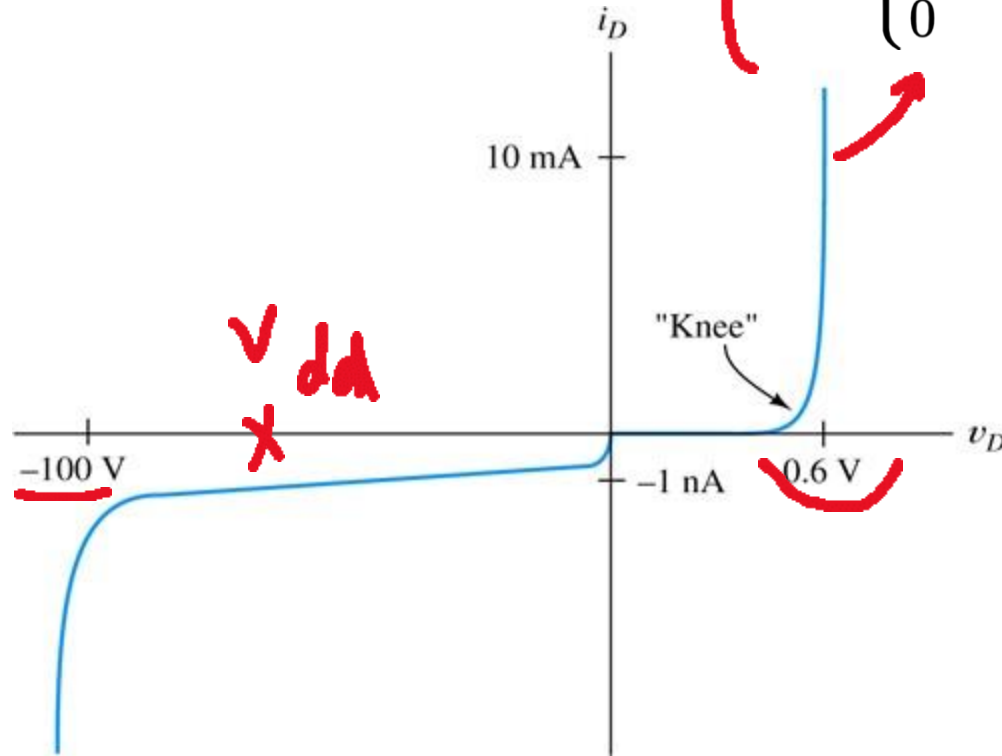
# I-V characteristics of a practical diode






$$i_D = \begin{cases} I_0 \left( e^{\frac{v_D}{nV_T}} - 1 \right) & v_D \geq 0 \\ 0 & v_D < 0 \end{cases}$$

# I-V Characteristics

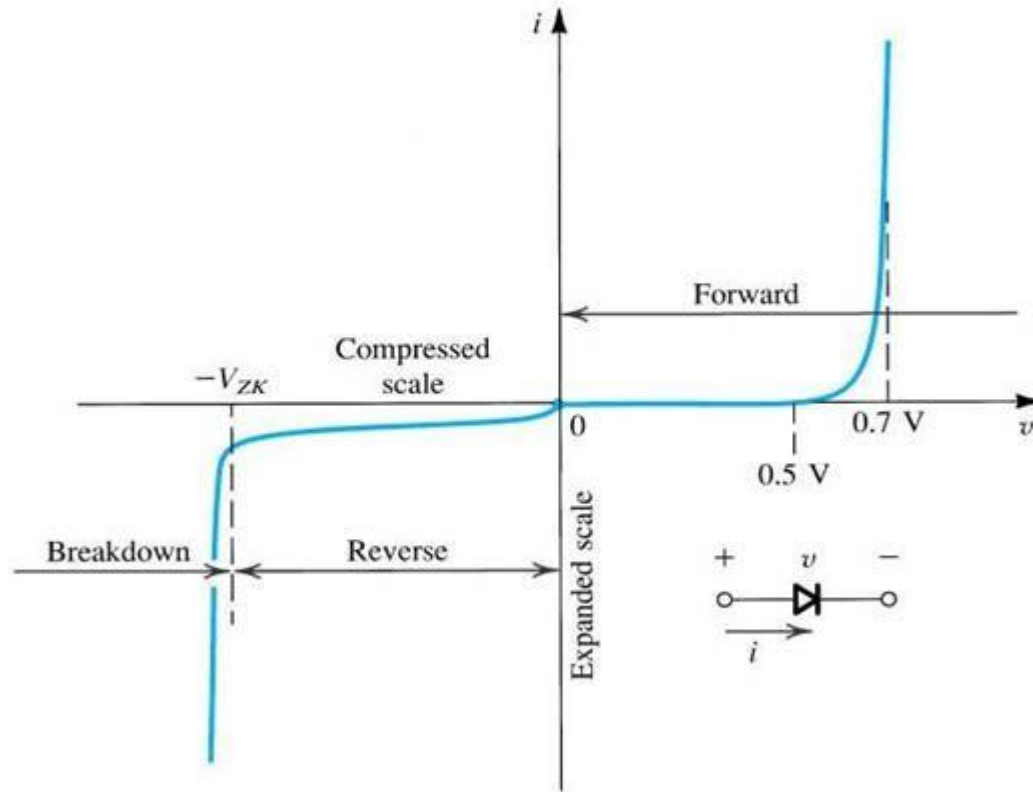

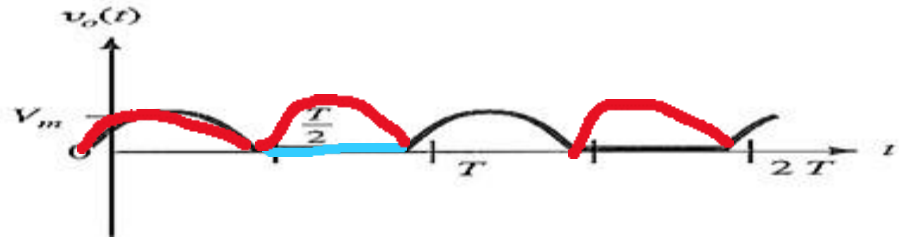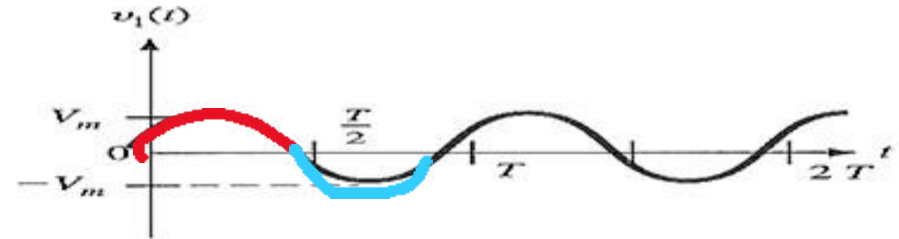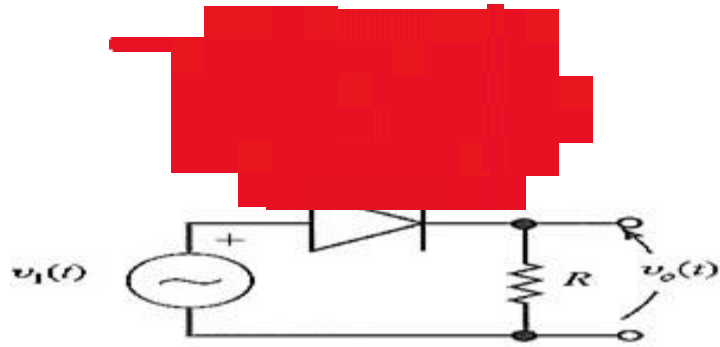
# Half-wave Rectification



- » Simplest process used to convert ac to dc.
- » A diode is used to clip the input signal excursions of one polarity to zero.





# Operational Amplifiers

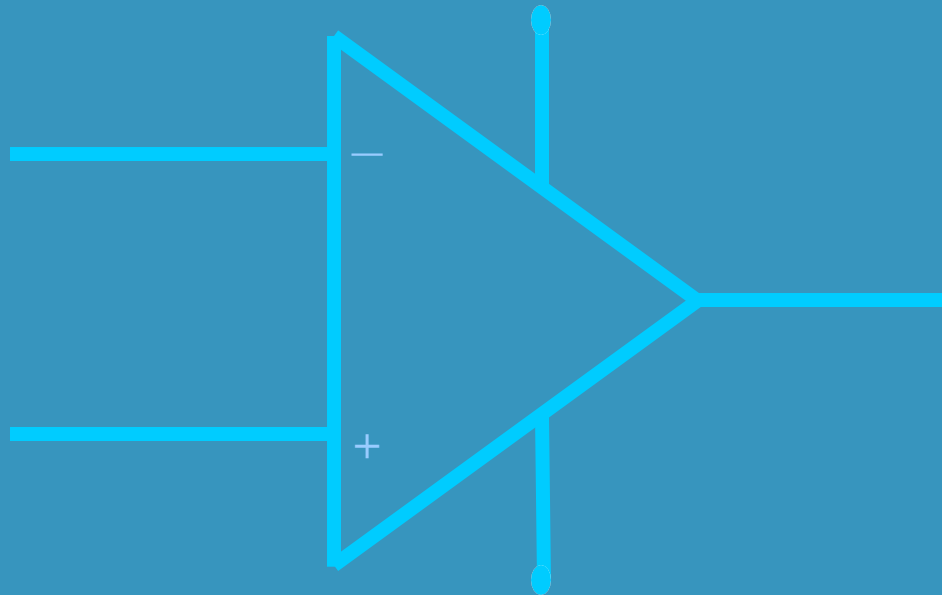

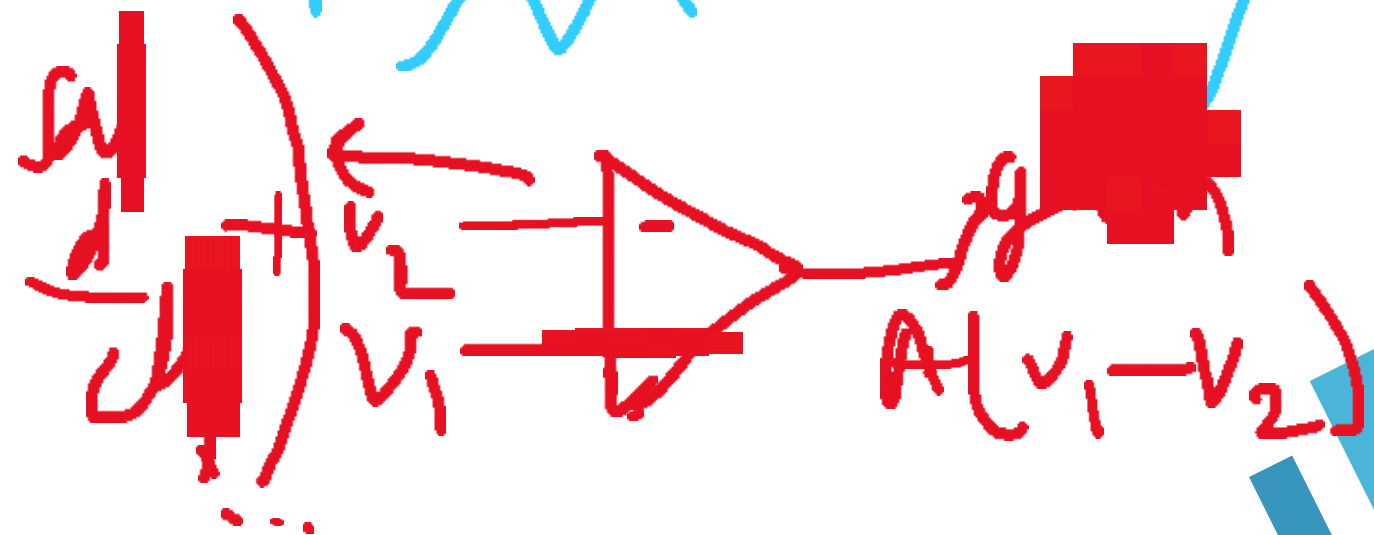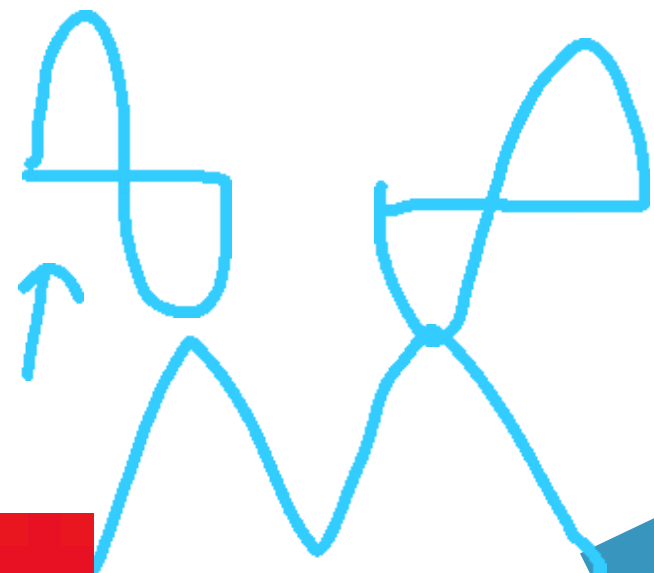

# Operational Amplifiers

- Usually Called Op Amps
- An amplifier is a device that accepts a varying input signal and produces a similar output signal with a larger amplitude.
- Usually connected so part of the output is fed back to the input. (Feedback Loop)
- Most Op Amps behave like voltage amplifiers. They take an input voltage and output a scaled version.
- The name “operational amplifier” comes from the fact that they were originally used to perform mathematical operations such as integration and differentiation..

# Operational Amplifiers

Op amps can perform operations of:-


- ❑ Adding signals
- ❑ Subtracting signals
- ❑ Integrating signals
- ❑ Differentiating signals

The applications of operational amplifiers ( shortened to op amp ) have grown beyond those listed above.

For example : Temperature sensor, Audio amplifiers, Active filters

# Pin Diagram of LM 741


Dual-In-Line or S.O. Package

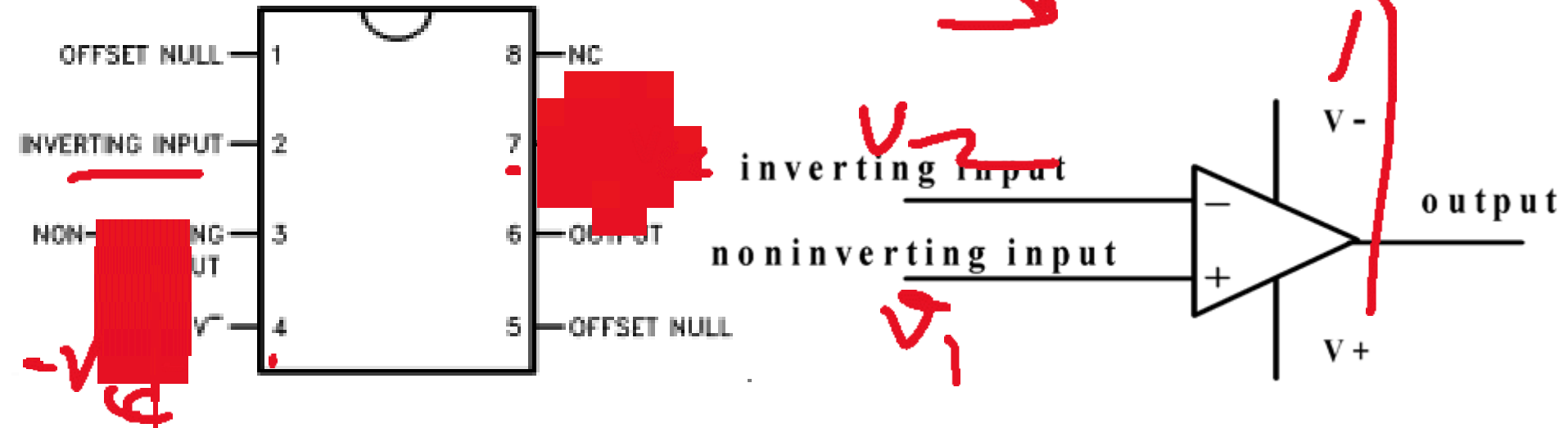


# Operational Amplifiers

A model of the op amp, with respect to the symbol

$$V_o = AV_d$$

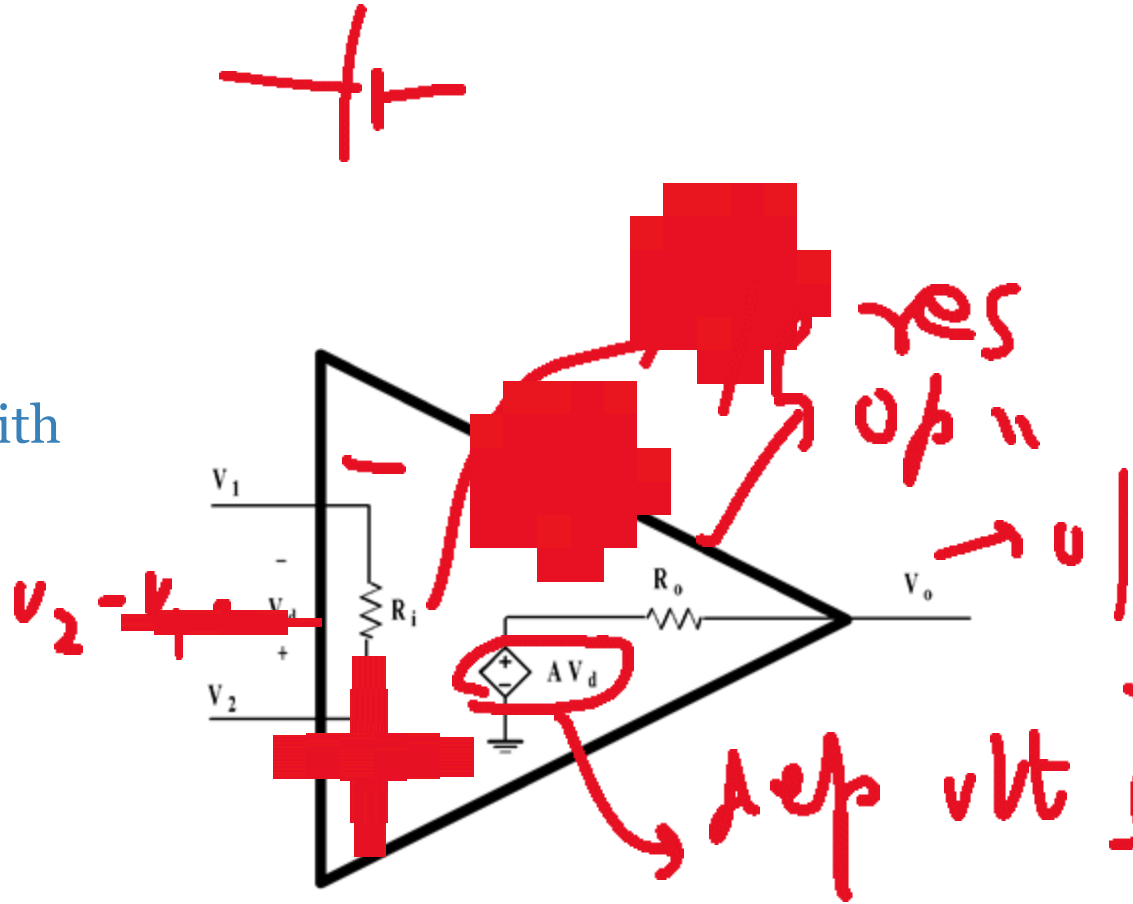

# Working circuit diagram of op amp.

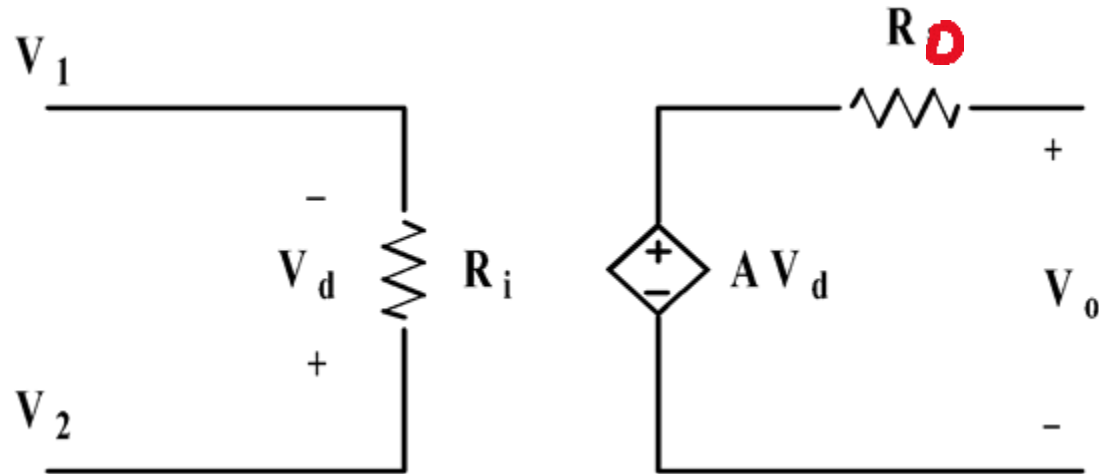

# Open Circuit Output Voltage


$$V_d = A v_d$$

	Voltage Range	Output Voltage
→ <b>Positive Saturation</b>	$A v_d > V^+$	<u><math>v_o \sim V^+</math></u>
→ <b>Linear Region</b>	$V^- < A v_d < V^+$	<u><math>v_o = A v_d</math></u>
→ <b>Negative Saturation</b>	<u><math>A v_d &lt; V^-</math></u>	<u><math>v_o \sim V^-</math></u>


The voltage produced by the dependent voltage source inside the op amp is limited by the voltage applied to the positive and negative rails.



## Voltage Transfer Characteristic

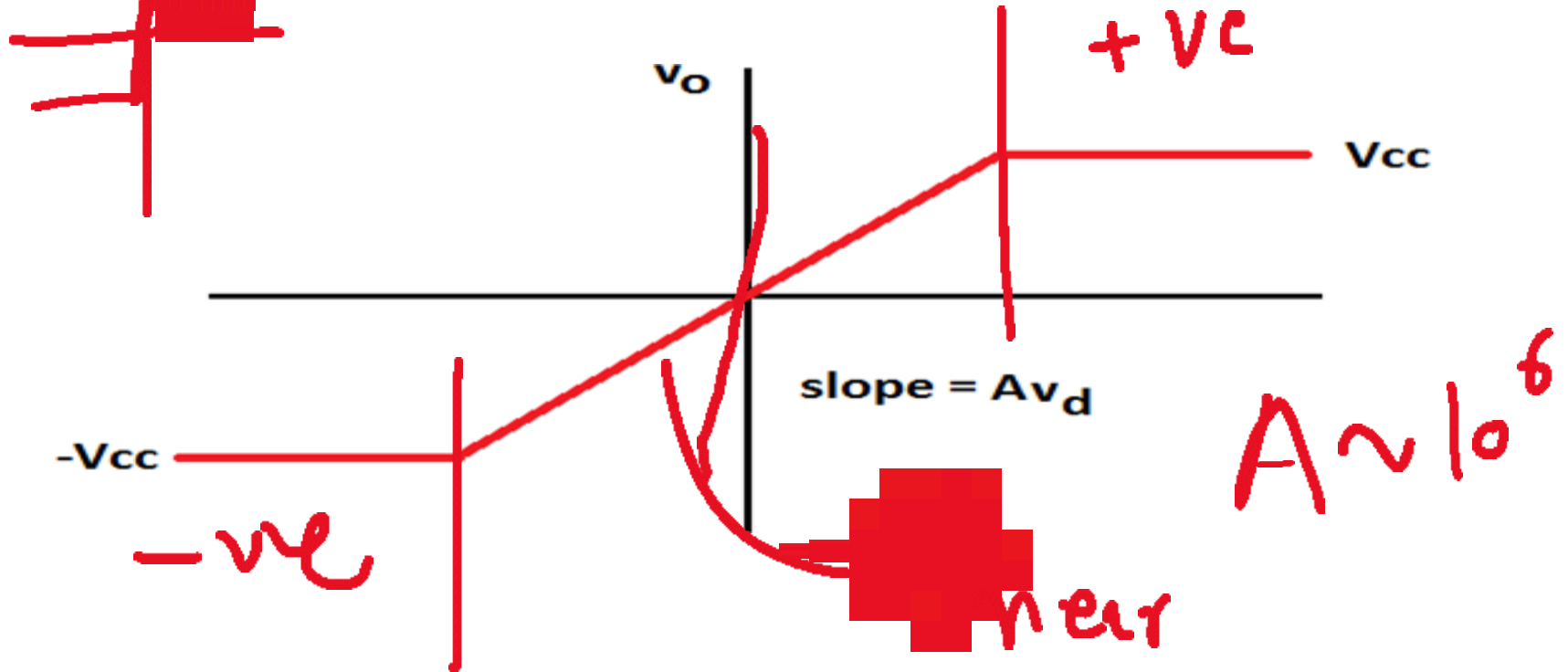

## Example: Voltage Comparator

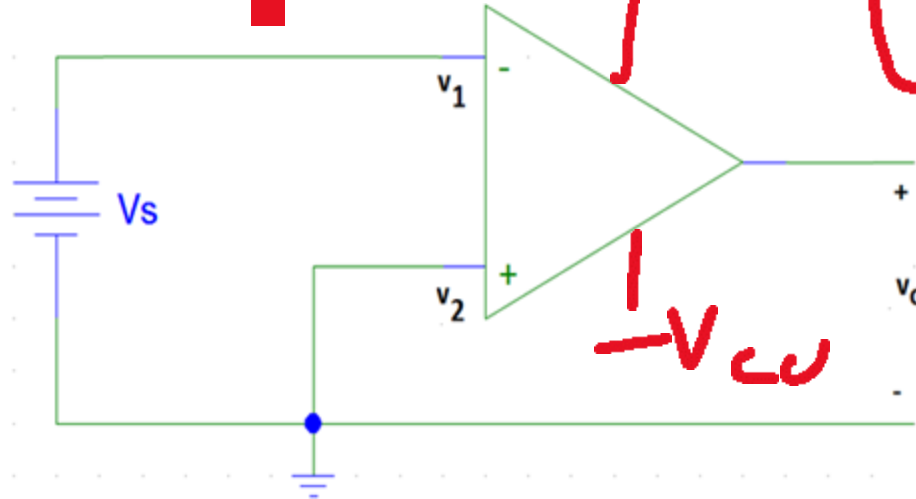

$$\left[ \begin{array}{l} V_1 < V_2 \\ V_1 < 0 \rightarrow A_{v_1} < -1 \end{array} \right]$$

When  $V_1$  is equal to  $V_2$ ,  $V_o = 0V$   
 When  $V_1$  is smaller than  $V_2$ ,  $V_o = V^+$ .  
 When  $V_1$  is larger than  $V_2$ ,  $V_o = V^-$ .

$$\left[ \begin{array}{l} V_1 > V_2 \\ V_1 > V_2 \end{array} \right] A_{v_1} > 1$$


# Electronic Response

Given how an op amp functions, what do you expect  $V_o$  to be if  $v_2 = 5V$ ,  $A=10$  when:


☐  $V_s = 0V$ ?

☐  $V_s = 5V$ ?

☐  $V_s = 6V$ ?

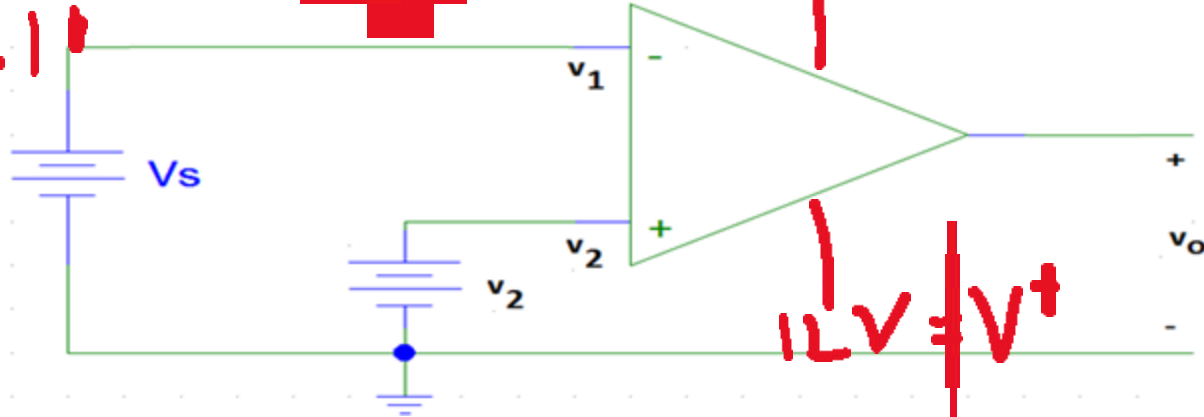


# Ideal Op Amp

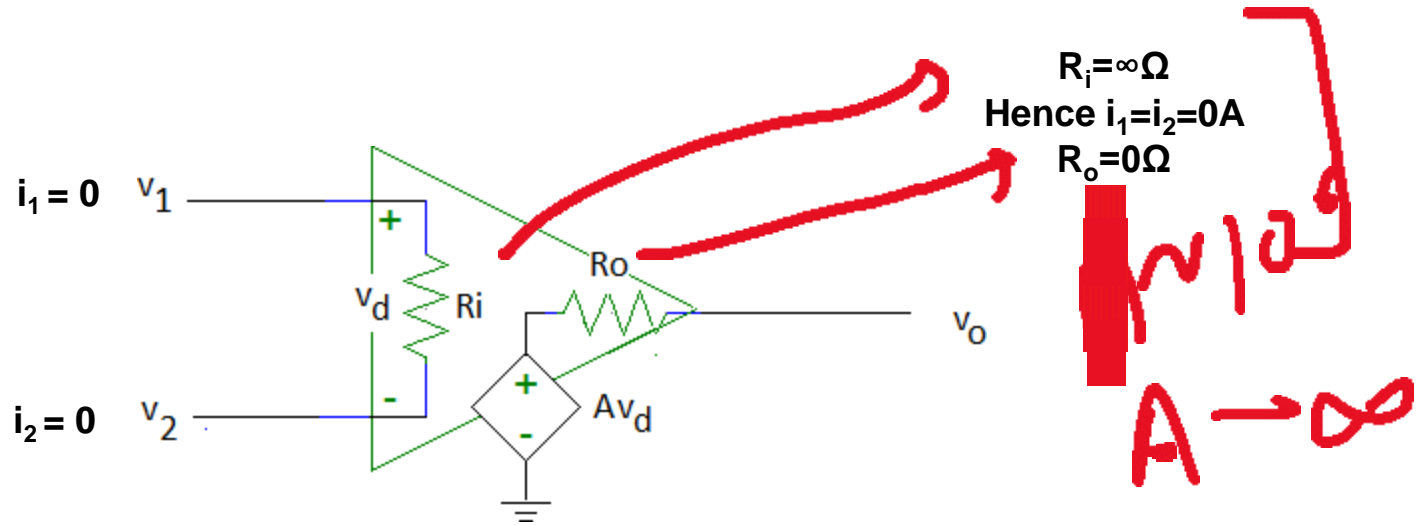


# FEEDBACK IN CIRCUITS

$V_o \uparrow \downarrow$

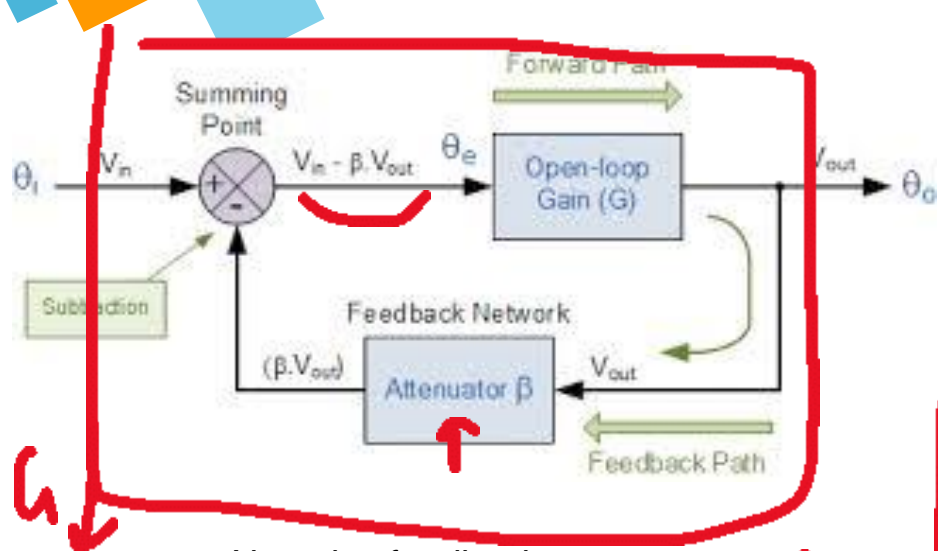

Negative feedback

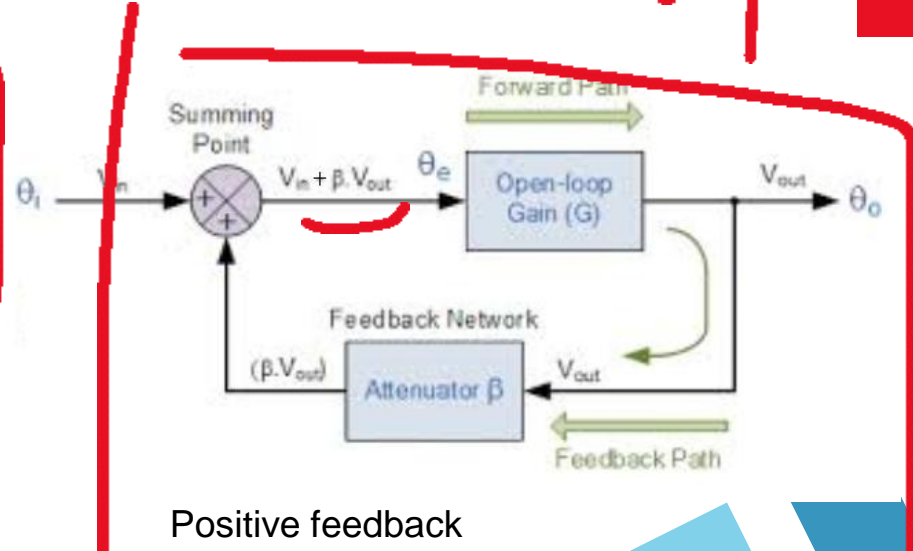


Positive feedback

$V_o \uparrow \downarrow$



# Why Negative Feedback?

- Gain of op amp (open loop gain) is of the order of  $10^6$  which is enough to drive the op amp into saturation.
  - We want the operation of op amp to be in the linear region for proper amplification purpose.
  - So to reduce gain we apply negative feedback.
- 

## Why positive feedback?

- » When we want the amplifier to work in saturation **only** then we use positive feedback.
- » It decreases the bandwidth and increases the overall amplification.
- »  $G_{pf} = A / (1 - AB)$

# Negative Feedback Equation

We see that the effect of the negative feedback is to reduce the gain by the factor of:  $1 + \beta G$ .  
This factor is called the “feedback factor” or “amount of feedback” and is often specified in decibels (dB) by the relationship of  $20 \log (1 + \beta G)$ .

System Gain,  $G = \frac{V_{out}}{V_{in}}$

$G$  = open loop voltage gain

$\rightarrow G \times V_{in} = V_{out}$

$\rightarrow G(V_{in} - \beta V_{out}) = V_{out}$

$G.V_{in} - \beta.G.V_{out} = V_{out}$

$G.V_{in} = V_{out}(1 + \beta G)$

$\beta$  is the feedback fraction

$\beta G$  = the loop gain





$1 + \beta G$  = the feedback factor

$\rightarrow \therefore \frac{V_{out}}{V_{in}} = Gv = \frac{G}{1 + \beta G}$   $Gv$  = closed loop voltage gain






## Applications of Negative Feedback:-

- Inverting Amplifier 
  - Non-Inverting Amplifier 
  - Adder , Subtractor 
  - Log , Antilog
  - Integrator, Differentiator
  - Temperature sensor
  - Instrumentation amplifier
  - Active Filters
- 

## Virtual Short Circuit in Ideal OpAmp

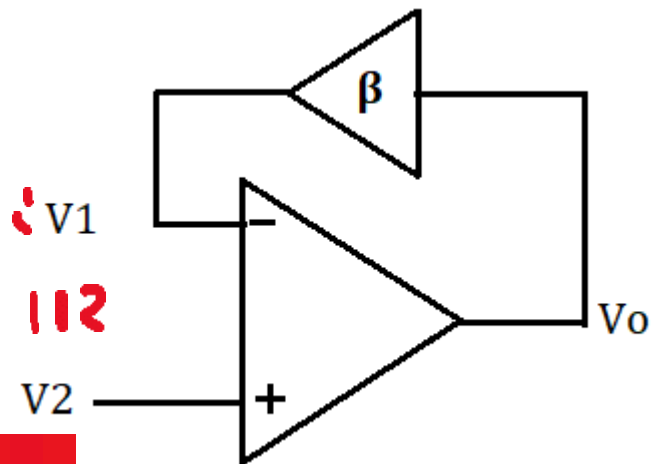

$$V_0 = A(V_2 - V_1)$$

$$\Rightarrow V_0 = A(V_2 - \beta V_0)$$

$$\Rightarrow V_0(1 + A\beta) = AV_2$$

$$\Rightarrow V_0 = \frac{AV_2}{1 + A\beta}$$

$$\text{as } A \rightarrow \infty, V_0 = \frac{V_2}{\beta}$$


$$\Rightarrow V_1 = \beta V_0 = V_2$$

$A \rightarrow \infty$

$$V_0 = \frac{V_2}{\beta + 1}$$

$V_A \uparrow$

## Inverting amplifier:

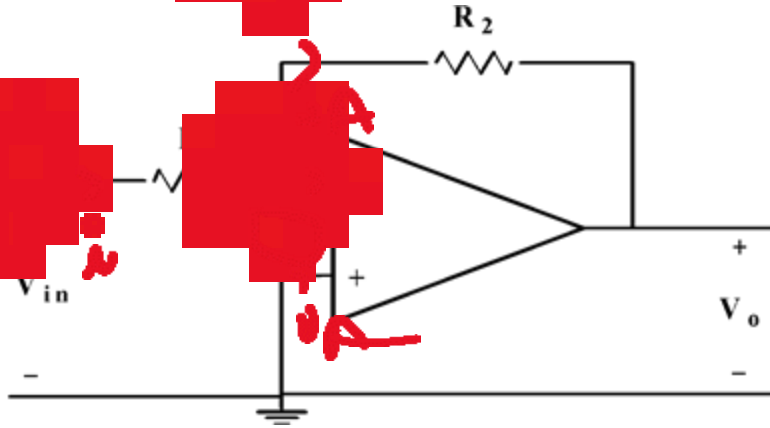


Writing a nodal  
equation at (a) gives;

$$i = \frac{V_{in} - V_i}{R_1} = \frac{V_i - V_o}{R_2}$$

With  $V_i = 0$  we have;

$$V_o = -\frac{R_2}{R_1} V_{in}$$

## Non-inverting Amplifier

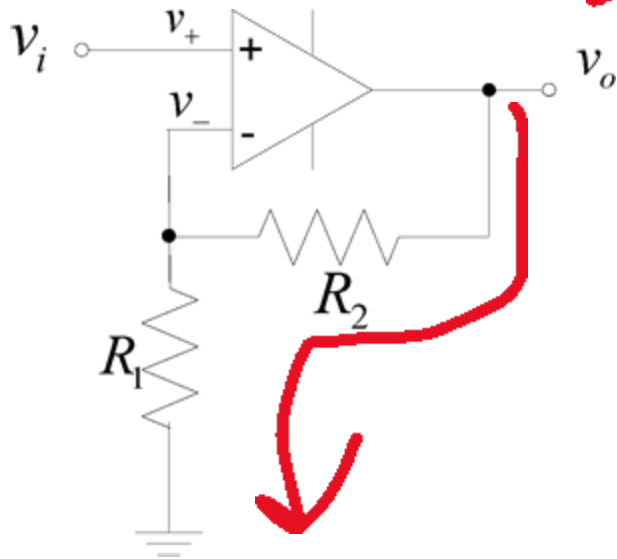

Closed-loop voltage gain  $A_F = \frac{v_o}{v_i}$

$$v_i = v_+ = v_- = \frac{R_1}{R_1 + R_2} v_o$$

$$A_F = \frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$

# Summing Amplifier



$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_0}{R_{fb}}$$

$$\rightarrow V_0 = - \left[ \left( \frac{R_{fb}}{R_1} \right) V_1 + \left( \frac{R_{fb}}{R_2} \right) V_2 \right]$$


If  $R_1 = R_2 = R_{fb}$  then,

$$V_0 = -[V_1 + V_2]$$


Therefore, we can add signals with an amp.

$$V_0 = -V_1 - V_2$$

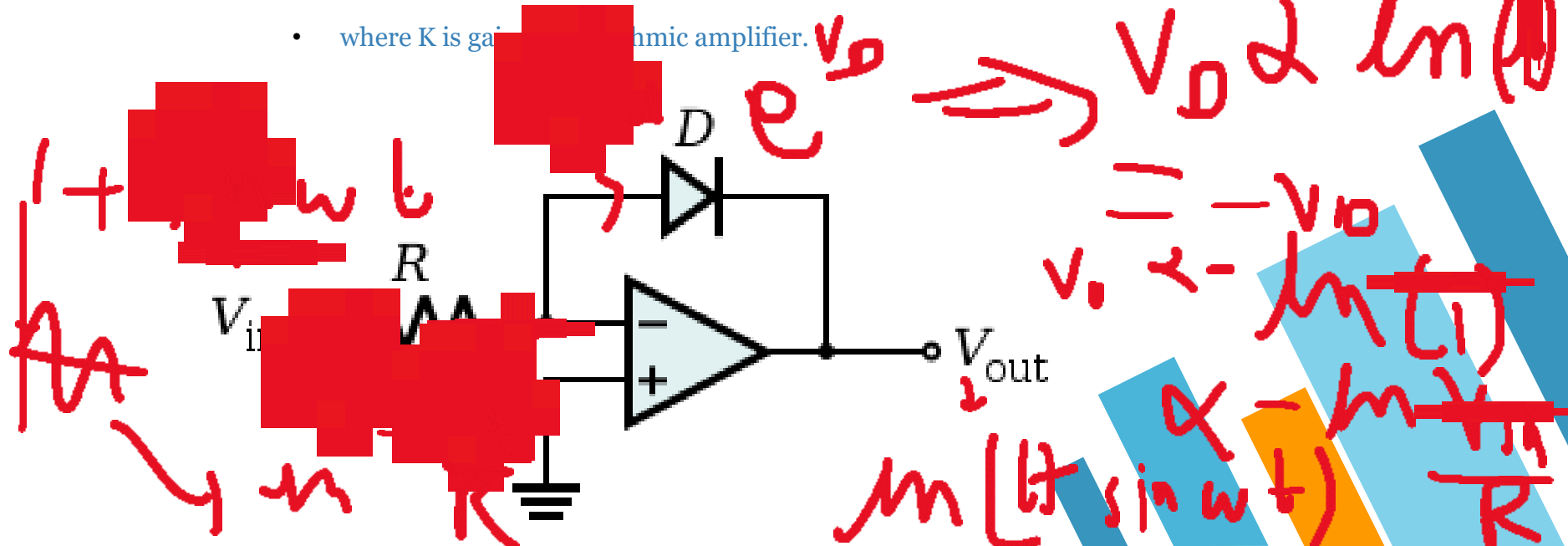- If  $V_i$  is the input signal then the output is  $V_o = K \ln(V_i)$
- where  $K$  is gain of the transimpedance amplifier.



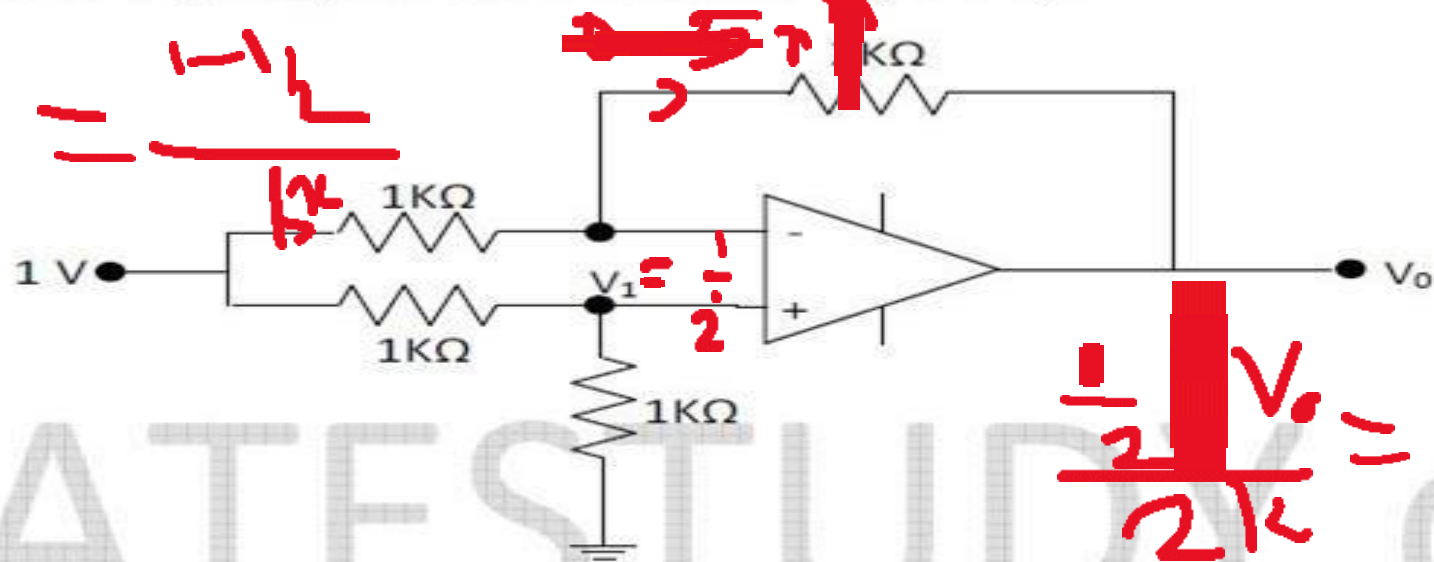For the Op-Amp circuit shown in the figure.  $V_0$  is




- 2 V
- 1 V

- c.  $-0.5\text{ V}$   
d.  $0.5\text{ V}$

$$\frac{\frac{1}{2} V_0}{2k} = 0.5 \text{ m}$$

## Questions

$$\frac{R_2}{R_1} \checkmark$$

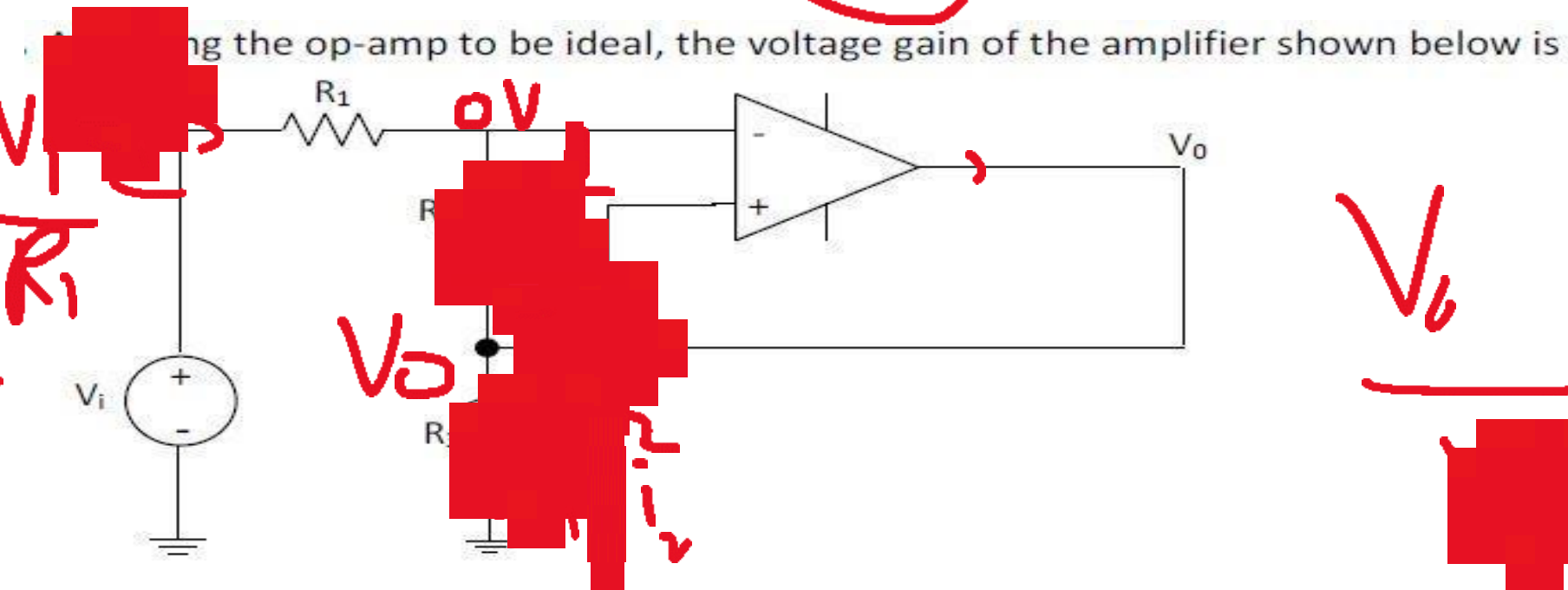


$$\frac{V_o}{V_i} =$$



## Questions

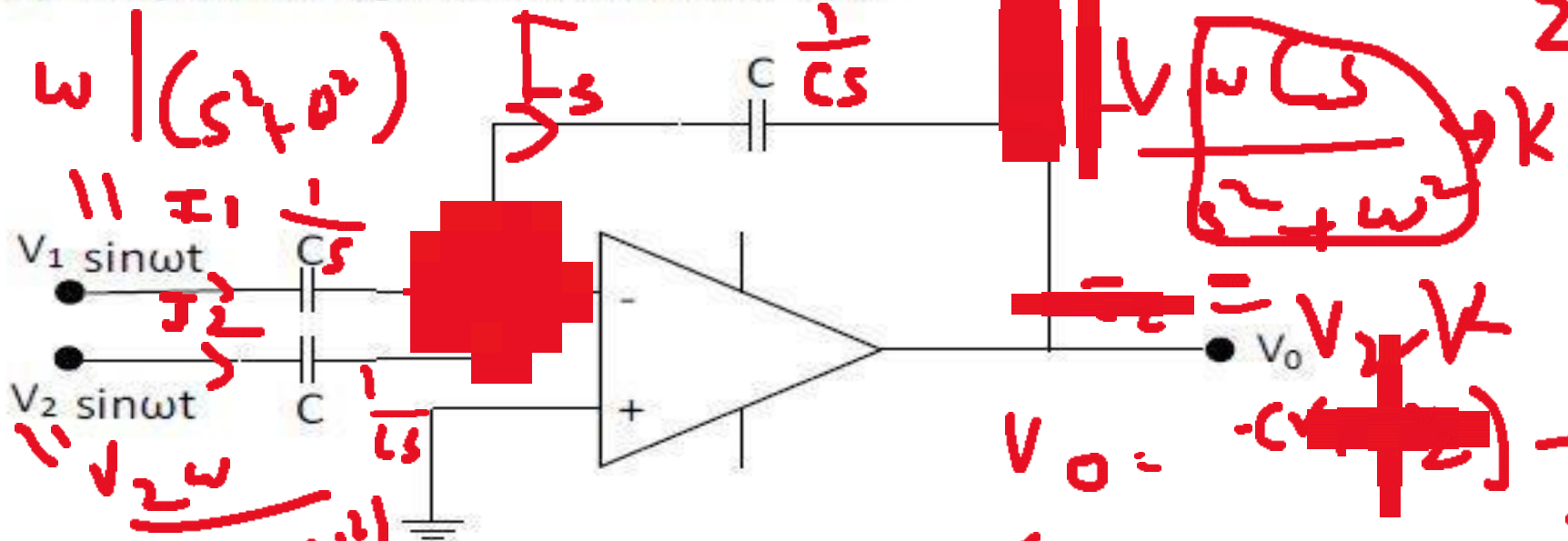1. If the op-amp in the figure, is ideal then  $V_0$  is



- a. Zero  
b.  $(V_1 - V_2) \sin \omega t$


- c.  $-(V_1 + V_2) \sin \omega t$   
d.  $(V_1 + V_2) \sin \omega t$

$$\frac{-V_0}{1/c_s} I_3 = I_1 + I_2 = (v_1 + v_2) k$$

$$V_0(s) = - (v_1 + v_2) \frac{\omega}{s^2 + \omega^2}$$
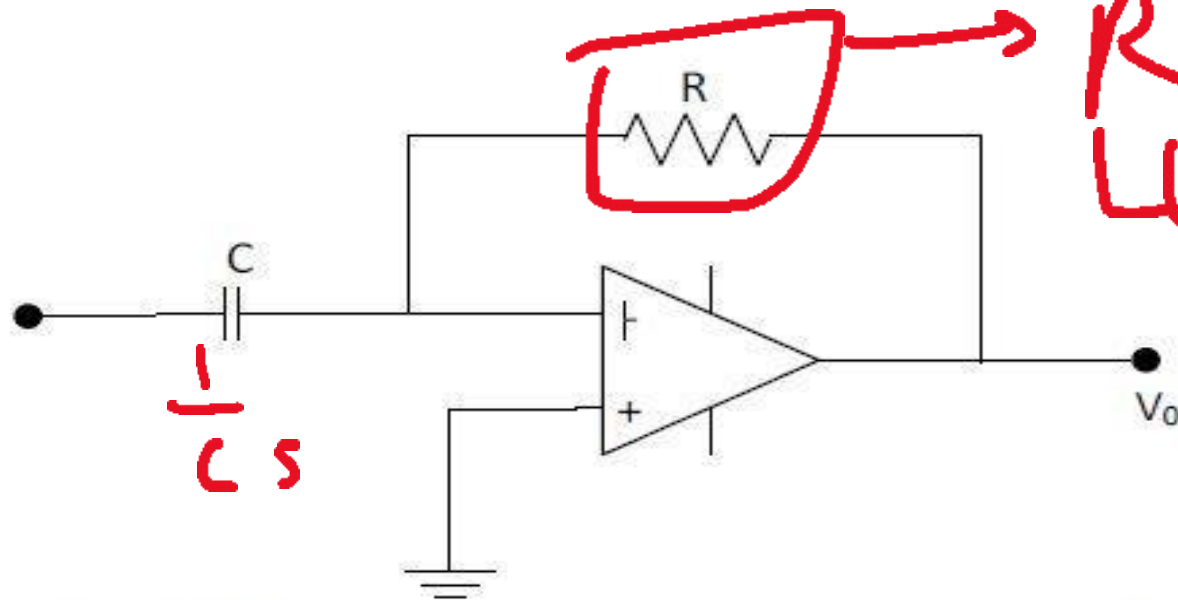
## Questions

Assume that the op-amp of the figure is ideal. If  $V_i$  is a triangular wave, then  $V_o$  will be




- a. square wave
- b. triangular wave

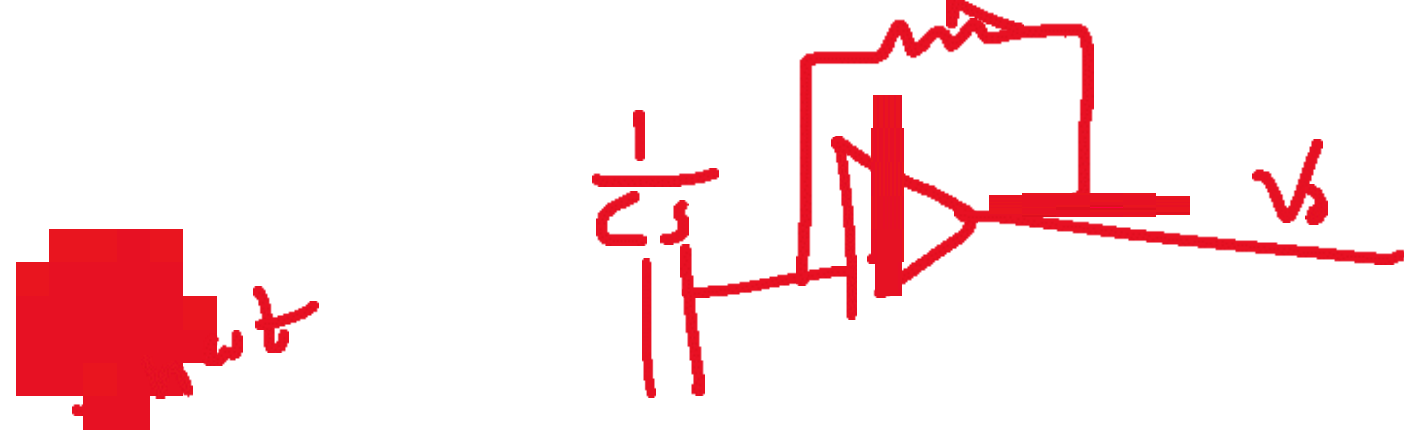- c. parabolic wave
- d. sine wave

$A \sin \omega t$

$R/(1/s) = s$   
 $s^2 \rightarrow \text{twice}$



cos wt

$$I = \frac{Cs \omega}{s^2 + \omega^2}$$

$$\rightarrow V_o = -$$

$$\frac{R\omega R}{1}$$

$$\frac{s}{s^2 + \omega^2}$$

$$V_o =$$

$$-R\omega \cos \omega t$$

## Alternate proof for virtual short circuit in Ideal OpAmp

In ideal OpAmp,  $R_i = \infty \Omega$  (approx), and currents in input terminals are zero, then potential difference between the terminals  $V_d = 0V$ , hence  $V_+ = V_-$





# Thank You!

Contact us:



**Mohit Shringi: 6377566533**

**Rishabh Borad: 9450336209**

**P. Shyam Prasad: 9494146711**

